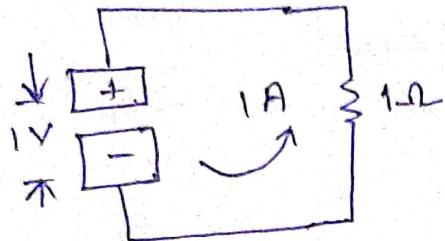


ESP

potential means difference



- electron always move from -ve side +ve side
- movement of electron is nothing but "current"
 - current always flows opposite direction to the flow of e^-

initially voltage find
 ↓
 current
 ↓
 Resistance

initially they found relation as

$$R = \frac{V}{I}$$

power is rate
 Energy is integral

V → Generation → voltage (V)

I → Transmission → current (A)

R → Utilization → Resistance (Ω)

P → power / sec → power (W)

E → cumulative
~~energy~~ power → Energy (W/s)

→ We feel the effect of current not voltage

(or)

shock due to the current not by voltage

Rating = No of e^-/sec



$$P = I^2 R$$

$$= I \cdot I \cdot R$$

$$\boxed{P = I V}$$

→ wire burning when more current flows through it i.e. greater than its rating

Let,

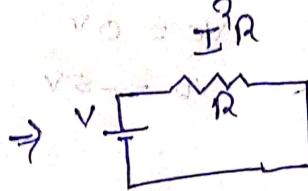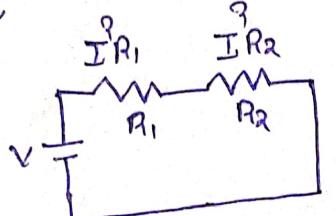


$$I^2 R = I^2 R_1 + I^2 R_2$$

$$I^2 R = I^2 (R_1 + R_2)$$

$$\therefore R = R_1 + R_2$$

Let

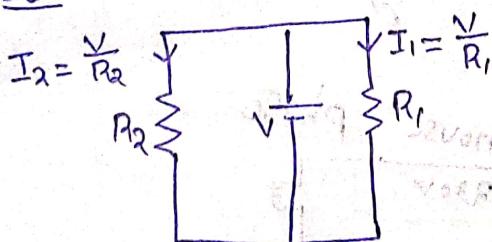

W.K.T
total power = sum of individual powers

$$\frac{V^2}{R} = \frac{V^2}{R_1} + \frac{V^2}{R_2} \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\boxed{R = \frac{R_1 R_2}{R_1 + R_2}}$$

$3\text{ero} \times \text{Anything} = 0$

$3\text{ero} \times \infty \neq 0$ (indeterminate)

Let,

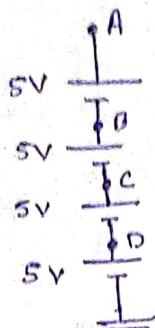


$$V_{AD} = 20\text{ V}$$

$$V_{BD} = 15\text{ V}$$

"

"

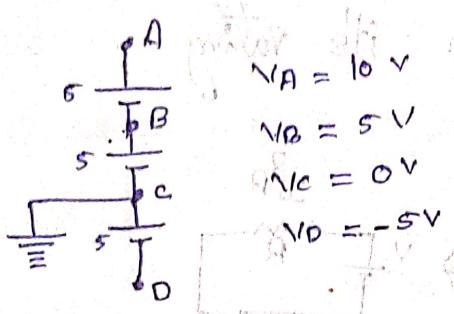

$$V_A = 10\text{ V}$$



$$V_B = 5\text{ V}$$

$$V_C = 0\text{ V}$$

$$V_D = -5\text{ V}$$

Ground \rightarrow Relative
Earth \rightarrow Absolute (always 0V)

Let

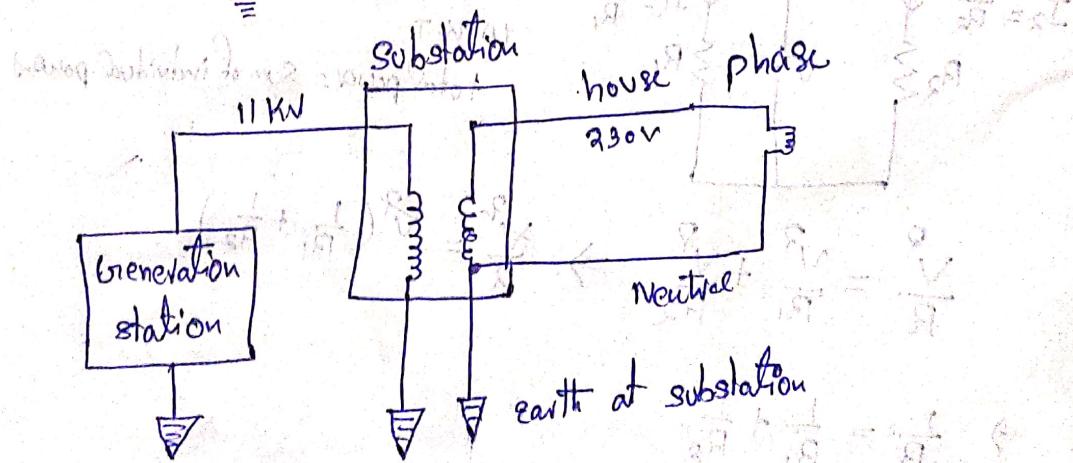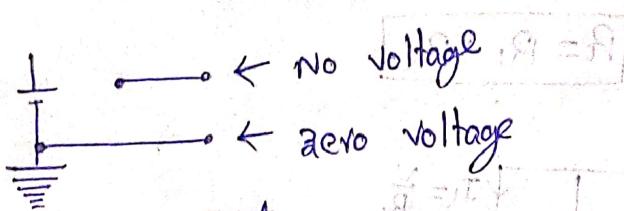

Ground \rightarrow common point


earth \rightarrow Absolute zero voltage

zero voltage \rightarrow connected to common point

No voltage \rightarrow not connected to anything
-ve voltage \rightarrow measure with common point

Electrical Fundamentals

①

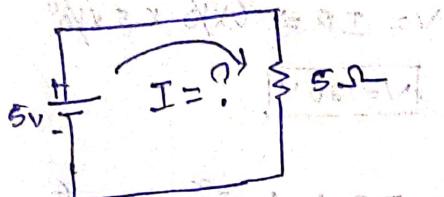

sol w.k.t

$$V = IR$$
$$I = \frac{V}{R} = \frac{5}{5} = 1$$
$$I = 1A$$

②




w.k.t

$$R = \frac{V}{I} = \frac{20}{5} =$$

$$R = 4\Omega$$

③

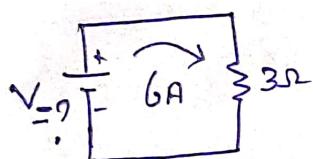


sol w.k.t

$$I = \frac{V}{R} =$$

$$V = IR \Rightarrow 6 \times 3 = 18$$

$$V = 18V$$

④

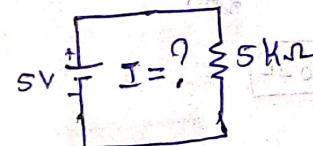

w.k.t

$$I = \frac{V}{R} = \frac{5}{5 \times 10^3}$$

$$I = 1mA$$

⑤



sol w.k.t

$$R = \frac{V}{I} = \frac{10}{5 \times 10^{-3}}$$

$$R = 2k\Omega$$

⑥




sol w.k.t

$$V = IR$$
$$= 2 \times 10^{-3} \times 6 \times 10^3$$

$$V = 12V$$

⑦

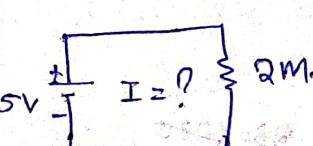


sol w.k.t

$$I = \frac{V}{R} = \frac{5}{2 \times 10^6}$$

$$I = 2.5 \mu A$$

⑧

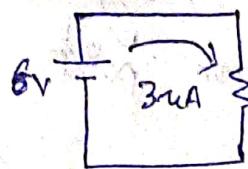


sol

W.K.T

$$R = \frac{V}{I} \Rightarrow \frac{6}{3 \times 10^{-3}} = 2000 \Omega$$

$$R = 2 \text{ k}\Omega$$

⑨

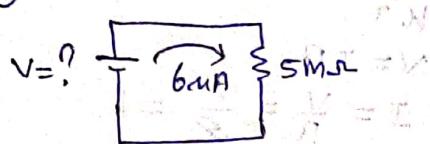


sol

W.K.T

$$V = IR \Rightarrow 6 \times 10^{-3} \times 5 \times 10^{-3}$$

$$V = 20 \text{ mV}$$

⑩

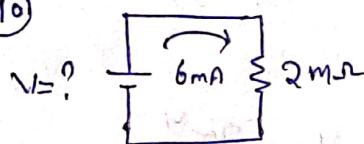


sol

$$V = IR \Rightarrow 6 \times 10^{-3} \times 2 \times 10^{-3}$$

$$V = 12 \text{ mV}$$

power law assessment

①

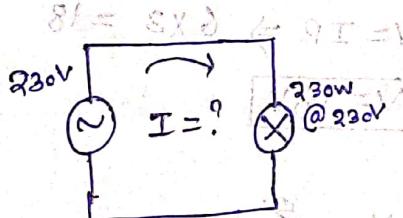

sol


W.K.T

$$P = \frac{V^2}{R}$$

$$P = \frac{V^2}{R} = \frac{230 \times 230}{230}$$

$$P = 230 \Omega$$

②

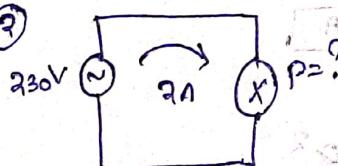

sol


W.K.T

$$P = VI$$

$$= 230 \times 2$$

$$P = 460 \text{ W}$$

③

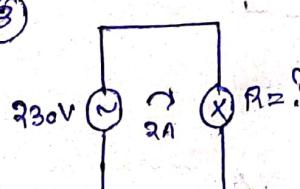


sol

$$W.K.T \quad R = \frac{V}{I} \Rightarrow \frac{230}{2} = 115$$

$$R = 115 \Omega$$

④

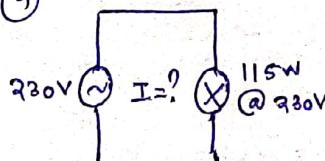

sol

To find I we need to find R

W.K.T

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{230 \times 230}{115}$$


$$R = 460 \Omega$$



$$I = \frac{V}{R} \Rightarrow \frac{220}{460\Omega} = 0.5$$

$$I = 0.5 A$$

Sol To find P first, need to find R

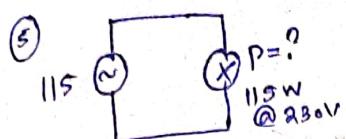


$$R = \frac{V^2}{P} = \frac{220 \times 230}{115} \Omega$$

$$R = 460 \Omega$$

$$I = \frac{V}{R} = \frac{115}{460} = 0.25$$


$$P = VI \Rightarrow 115 \times 0.25 \Rightarrow 28.75$$

$$P = 28.75 W$$

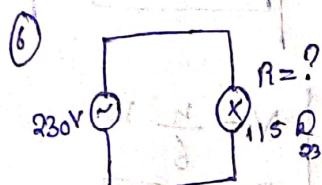

Sol above W.K.T

$$P = 460 \Omega$$

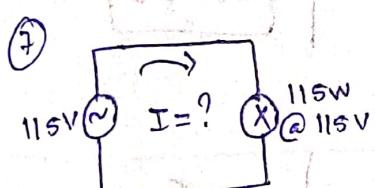


Sol To find I we need to find R

$$R = \frac{V^2}{P} = \frac{115 \times 115}{115} = 115 \Omega$$

$$R = 115 \Omega$$

$$I = \frac{V}{R} \Rightarrow \frac{115}{115} = 1$$

$$I = 1 A$$

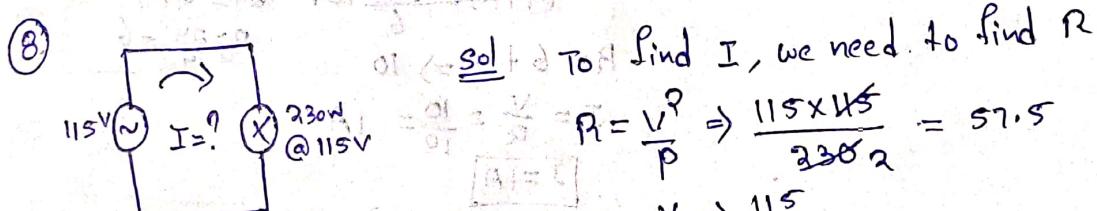


Sol To find I , we need to find R

$$R = \frac{V^2}{P} \Rightarrow \frac{115 \times 115}{230} = 57.5 \Omega$$


$$I = \frac{V}{R} \Rightarrow \frac{115}{57.5}$$

$$I = 2 A$$

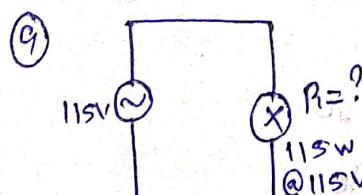

$$\underline{\text{Sol}} \quad R = \frac{V^2}{P} \Rightarrow \frac{115 \times 115}{115}$$

$$R = 115 \Omega$$

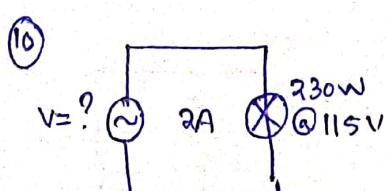


Sol To find V , first find R

$$R = \frac{V^2}{P} = \frac{115 \times 115}{230} = 57.5 \Omega$$

$$V = IR \Rightarrow 2 \times 57.5$$


$$V = 115 V$$

Service circuit Assessment

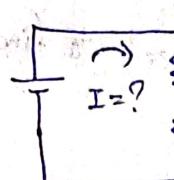① 


Sol. To find I ,
To find R
 $R = 3\Omega + 2\Omega$
 $R = 5\Omega$

$I = \frac{V}{R} \Rightarrow \frac{5}{5} = 1 \text{ A}$

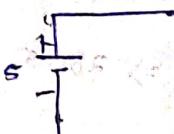② 


Sol. To find V_2
Voltage divider rule
 $V_2 = \frac{3}{(3+2)} \times 5$

$V_2 = 2 \text{ V}$

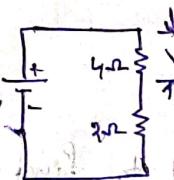③ 

Sol. To find V_1 ,
Voltage divider rule
 $V_1 = \frac{4}{(4+2)} \times 10$

$V_1 = 6.6 \text{ V}$

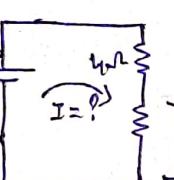④ 


Sol. To find I ,
Find TOTAL R
 $R_{\text{tot}} = \frac{4}{(4+6)} \times 10$

$(4+6) = \frac{4}{6} \times 10$


$P = 6 + 4 \Rightarrow 10$

$I = \frac{V}{R} = \frac{10}{10} = 1 \text{ A}$

$I = 1 \text{ A}$

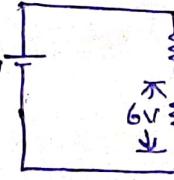⑤ 


Sol. To find R_2 ,
Voltage divider rule above
 $R = 6 \Omega$

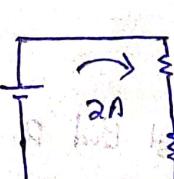⑥ 

Sol. $R = 4+6 \Rightarrow 10 \Omega$


$V = IR \Rightarrow 2 \times 10$

$V = 20 \text{ V}$

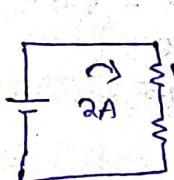⑦ 

Sol. To find V
W-K-T.
 $I = 2$
 $V_1 = I_1 \times R_1$
 $V_1 = 2 \times 4 = 8$

$V = V_1 + V_2$

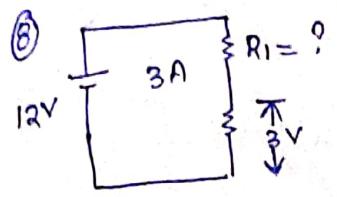


sol

w.k.t $V = V_1 + V_2$
 $I_2 = V_1 + 3$
 $V_1 = 12 - 3 \Rightarrow 9$

By ohm's law
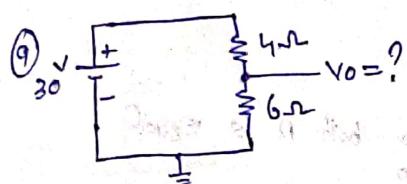
$$R = \frac{V}{I} \Rightarrow \frac{9}{3} = 3\Omega$$




sol To find V_o

w.k.t $I = \frac{V}{R} = \frac{30}{10} = 3A$

$V_1 = IR \Rightarrow 3 \times 4 = 12$

$V_o = V - V_1$
 $= 30 - 12$

$\boxed{V_o = 18V}$

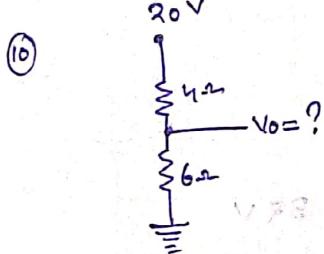

sol To find V_o


w.k.t $I = \frac{V}{R} = \frac{20}{10} = 2A$

$V_1 = 2 \times 4 = 8V$

$V_o = 20V - V_1 \Rightarrow 20 - 8$

$\boxed{V_o = 12V}$


parallel circuit assessment

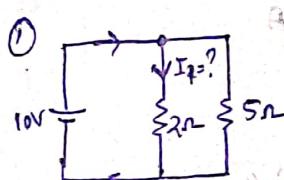

sol To find I_a

w.k.t at Node $V = 10V$

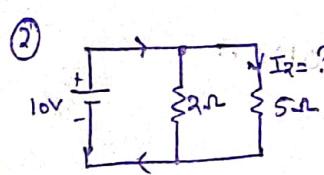
$$I_a = \frac{V}{R} = \frac{10}{2} = 5A \Rightarrow \boxed{I_a = 5A}$$



sol To find I_a

w.k.t at Node $V = 10V$
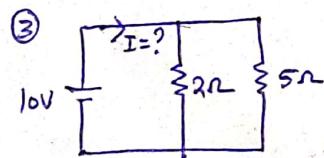
$$I_a = \frac{V}{R} = \frac{10}{5} = 2A \Rightarrow \boxed{I_a = 2A}$$



sol w.k.t


$$I = I_1 + I_2$$

$$= 5A + 2A$$

$$I = 7A$$

(or)

$$I = \frac{V}{R} = \frac{10}{1+2} = 7$$

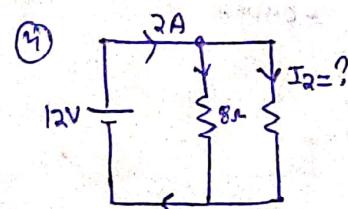

sol at Node $V = 12$







$$I_1 = \frac{12}{8} = 1.5$$









$$I = I_1 + I_2$$


$$I_2 = I - I_1 \Rightarrow 2 - 1.5$$

$$\boxed{I_2 = 0.5A}$$



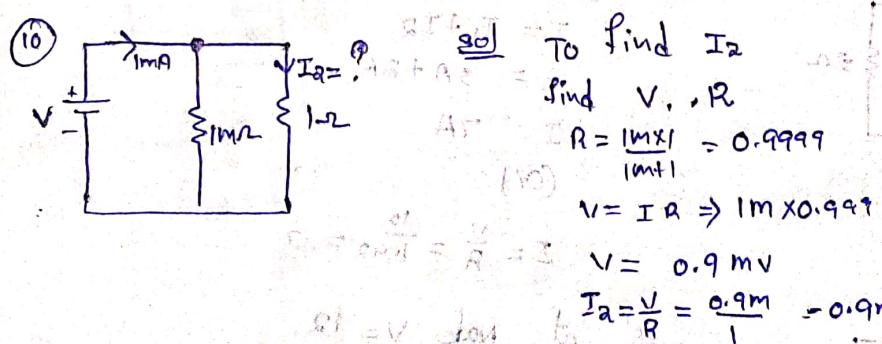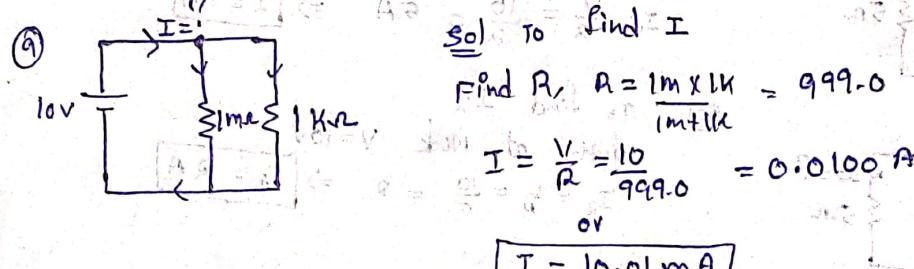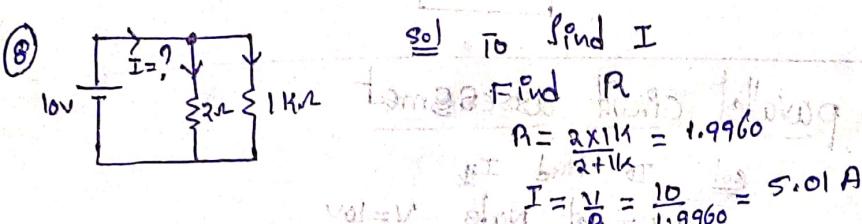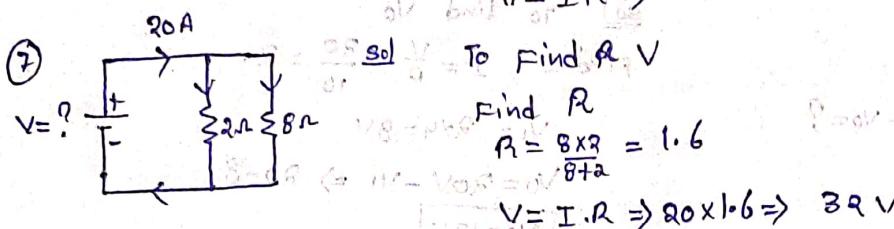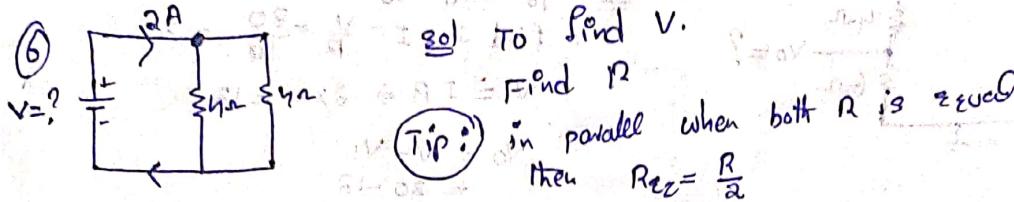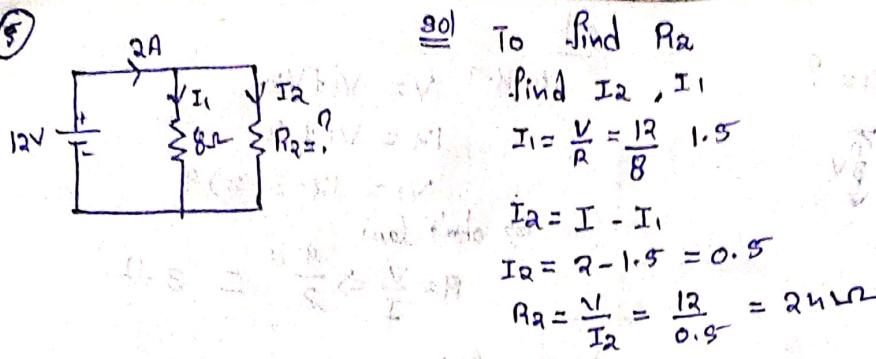

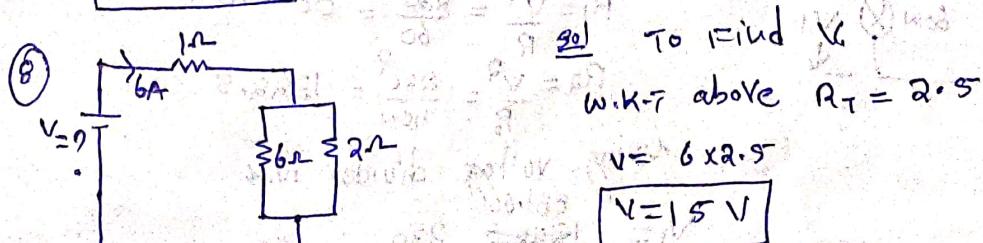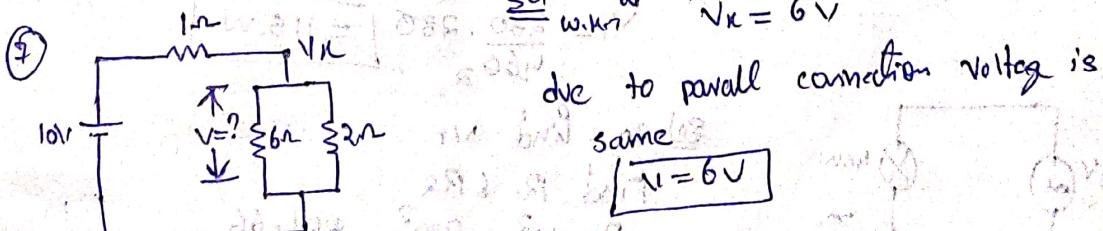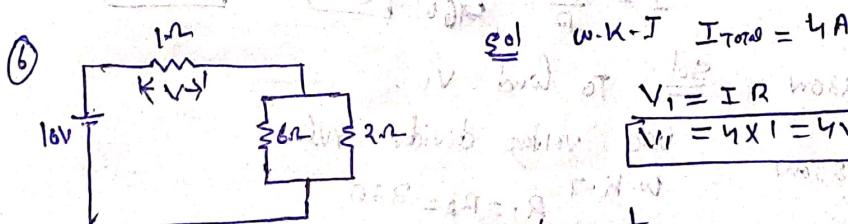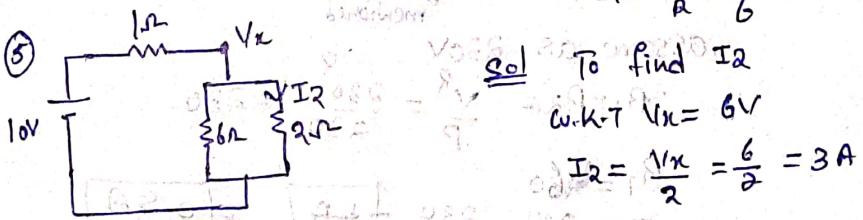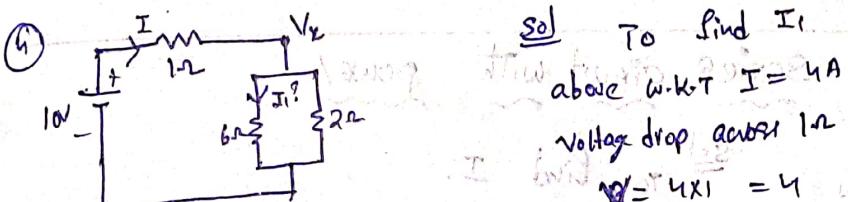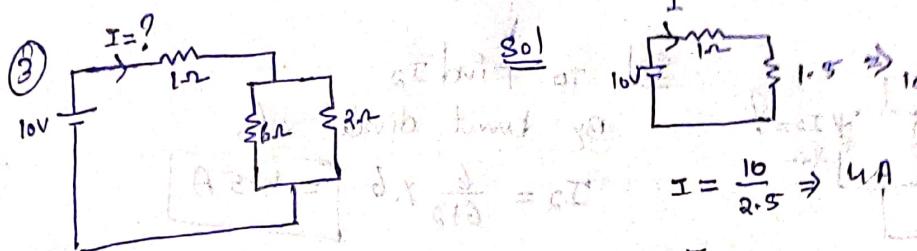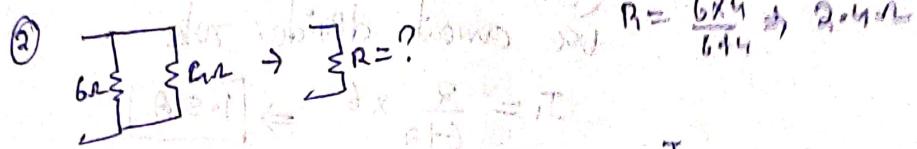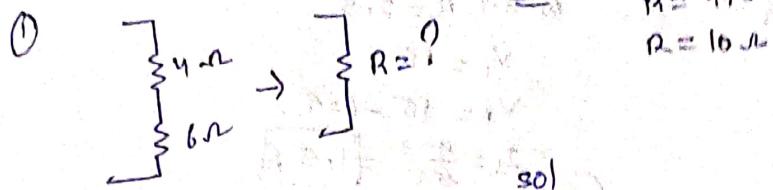

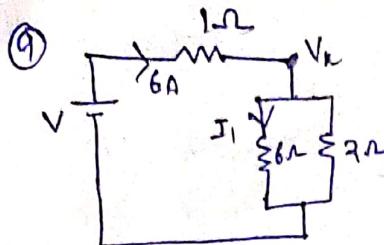

Sol To find I_1

Find V_{total} , V_L , R_T

W.K.T $R_T = 2 \cdot 5$


$V_T = 15$

$V_L = 15 - 6 = 9$

$I_1 = \frac{9}{8} = 1.125 \text{ A}$

(Q) Use current divider rule
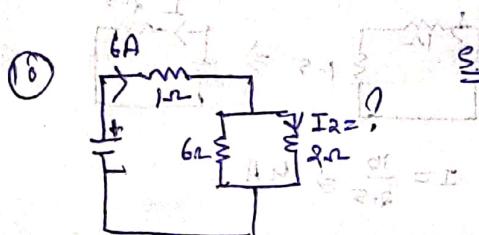
$$I_1 = \frac{2}{6+2} \times 6 \Rightarrow 1.125 \text{ A}$$






Sol To find I_2

By current divider rule

$I_2 = \frac{6}{6+2} = 4.5 \text{ A}$


Seriess circuit with power.

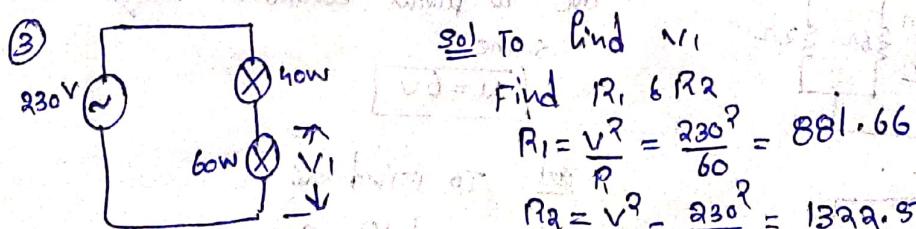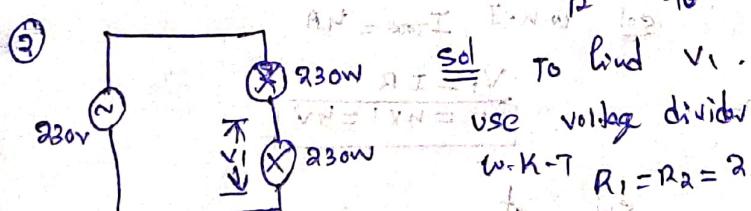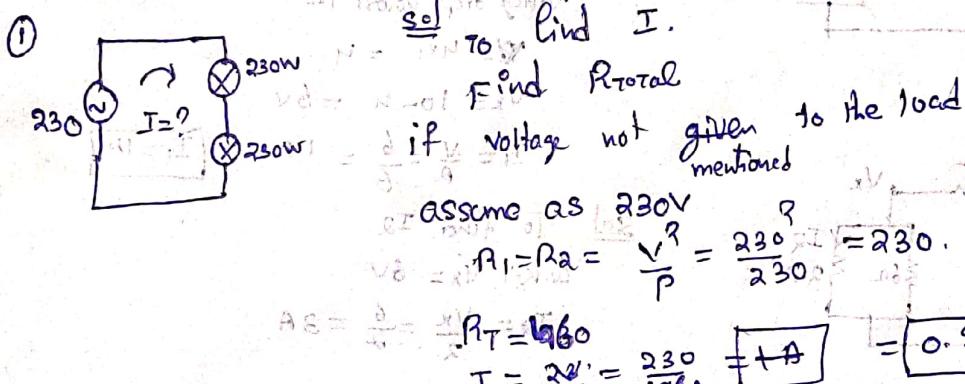

Using voltage divider rule

$$V_1 = \frac{881.66}{881.66 + 1322.5} \times 230$$


$$V_1 = 91.99 \text{ V}$$

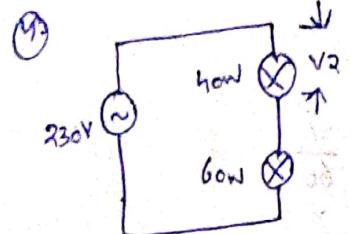

Sol To find V_2
use voltage divider rule

$$V_2 = \frac{1322.5}{2204.16} \cdot 230$$

$$V_2 = 138$$

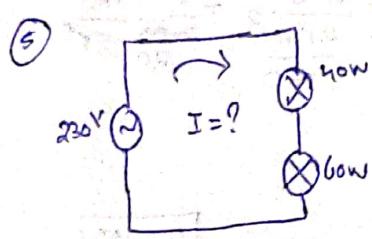


Sol To find I , first find R_{total}

w.k.t. $R_1 = 881.66$
 $R_2 = 1322.5$

$$R_T = 2204.16$$

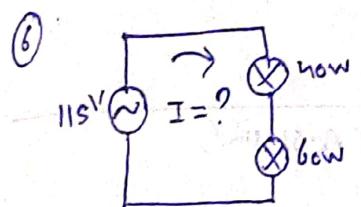
$$I = \frac{V}{R_T} = \frac{230}{2204.16} = 0.1A$$



Sol To find I .

w.k.t. $R_T = 2204.16$
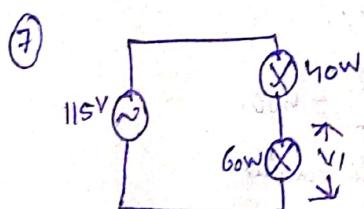
$$I = \frac{V}{R_T} = \frac{115}{2204.16} = 0.05A$$




Sol To find V_1

w.k.t. $R_1 = 881.66$ $R_T = 2204.16$
 $R_2 = 1322.5$


By using voltage divider rule
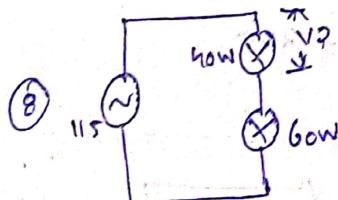
$$V_1 = \frac{881.66}{2204.16} \times 115 = 46V$$



Sol By using voltage divider rule
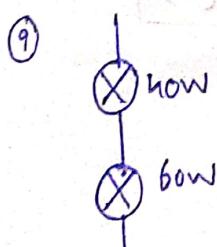
$$V_2 = \frac{1322.5}{2204.16} \times 115 = 69$$



Sol To find P

w.k.t. $R_1 = \frac{V^2}{P} = 881.66$

$R_2 = \frac{V^2}{P} = 1322.5$


$$R_T = R_1 + R_2 = \frac{V^2}{60} + \frac{V^2}{40} = \frac{2V^2 + 3V^2}{120}$$

$$R_T = 2204.16$$


$$P = \frac{V^2}{R_T} = \frac{5V^2}{120}$$

$$P = \frac{V^2}{5V^2} \cdot 120$$


$$P = \frac{120}{5} = 24W$$

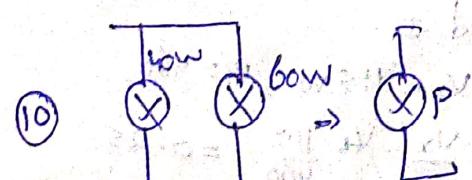

Sol w.k.t.

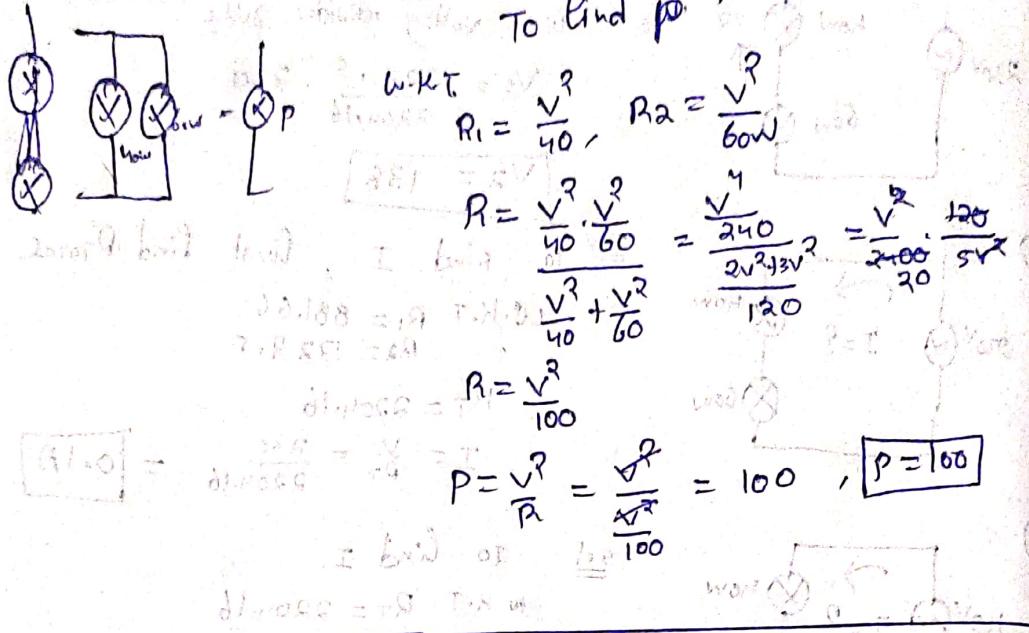

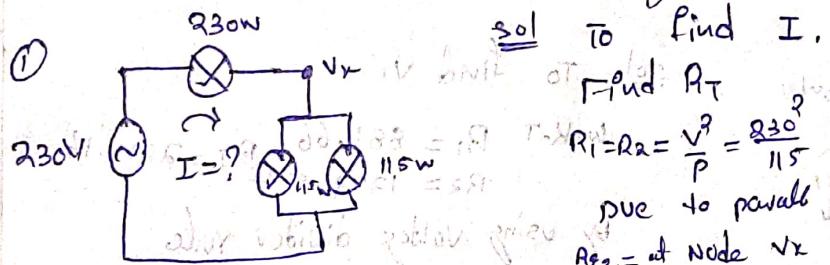Ques 2 = Series circuit using power (Ammeter)



$$V_x = 230 - 115 = 115$$


$$R_2 = 230 \Omega$$

$$R_3 = \frac{V^2}{P} = \frac{230^2}{230} = 230$$


$$R_T = R_3 + R_{eq}$$






$$= 460$$
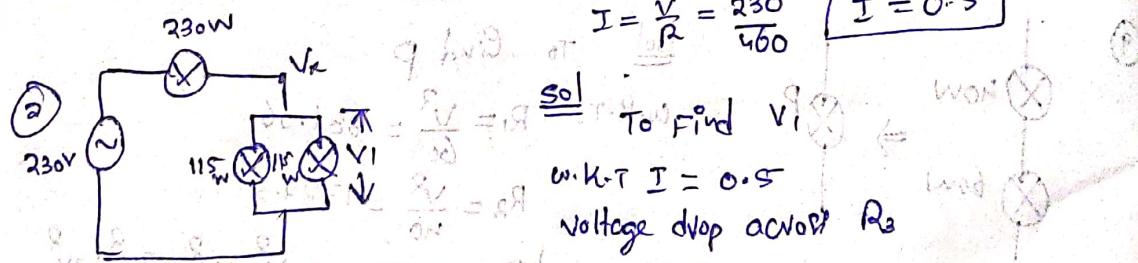
$$I = \frac{V}{R} = \frac{230}{460} = 0.5$$




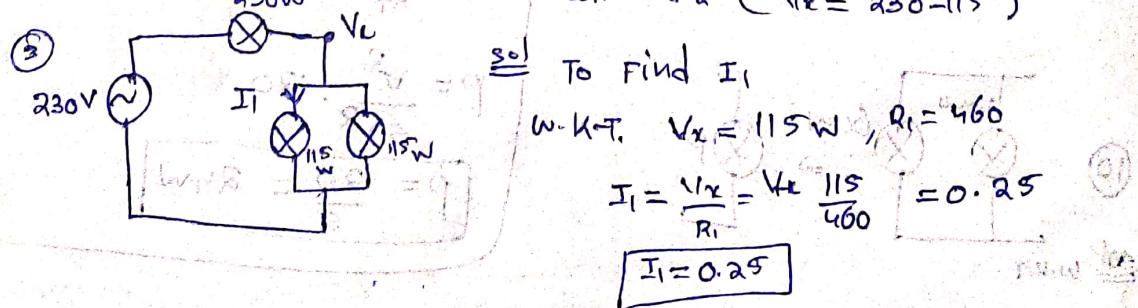Due to parallel connection 115 appears both sides ($V_x = 230 - 115$)



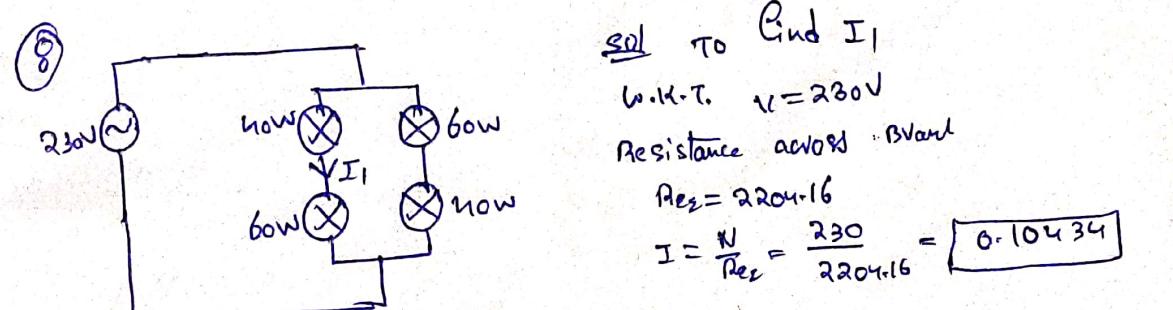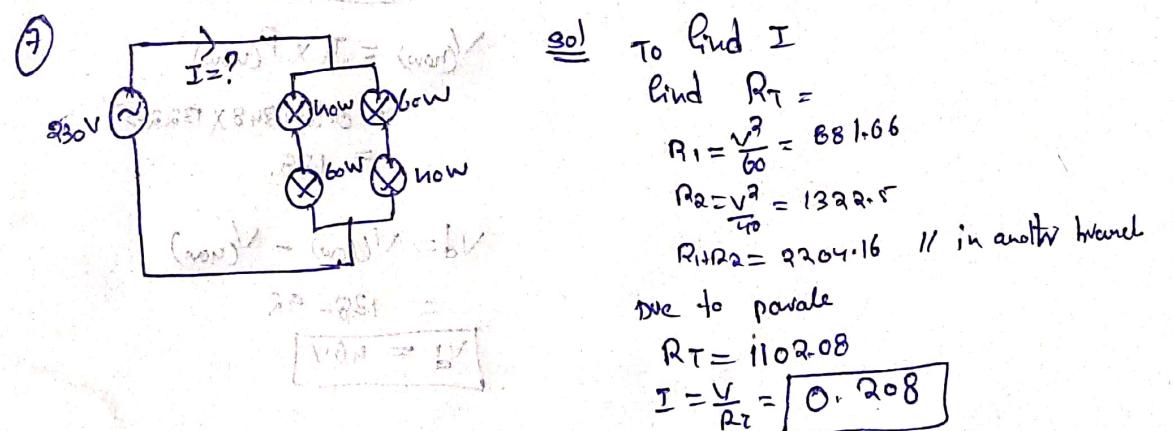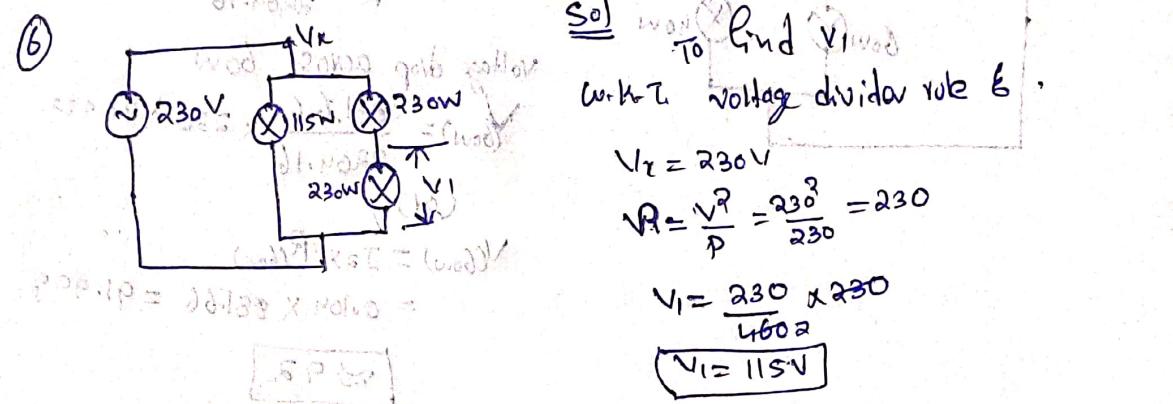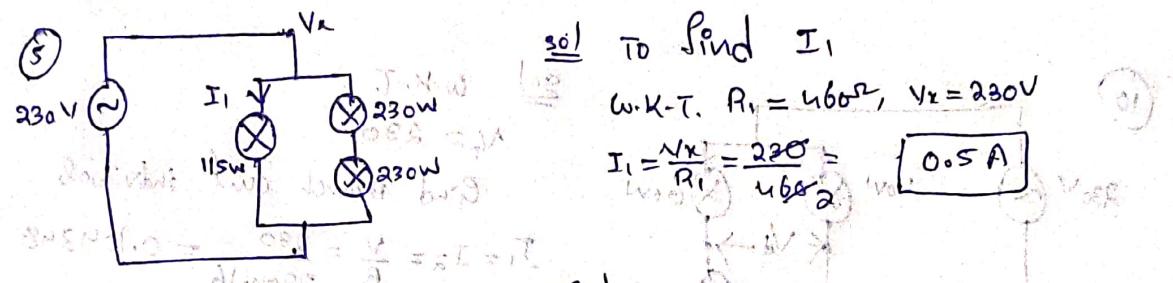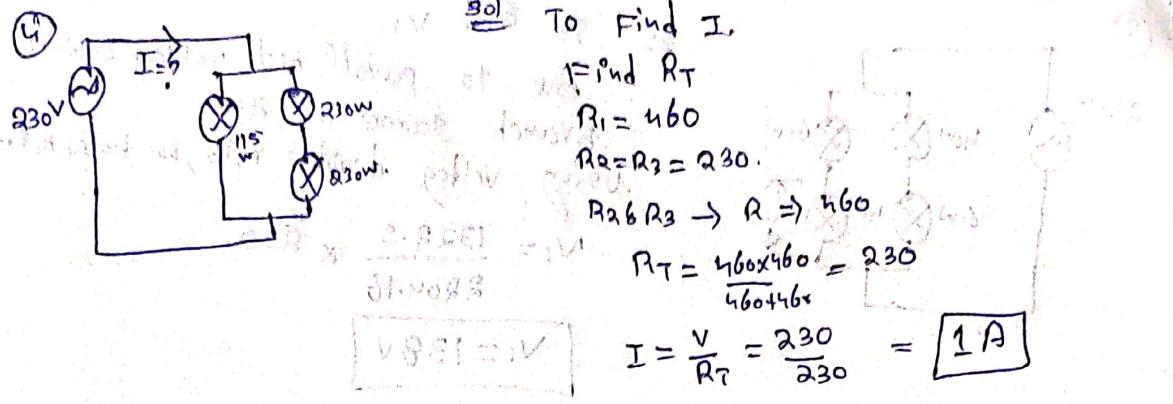

(9)

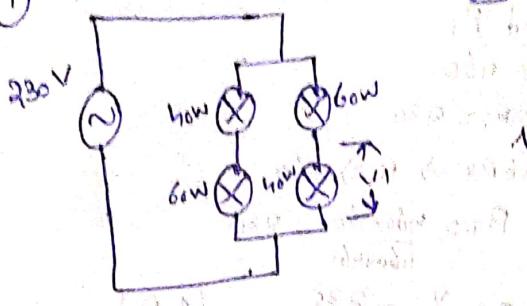


To find V_1
due to power cut voltage across
branch same i.e. 230V
using voltage divider rule, we know $P_{1322.5}$

$$V_1 = \frac{1322.5}{2204.16} \times 230$$

$$V_1 = 138V$$

(10)

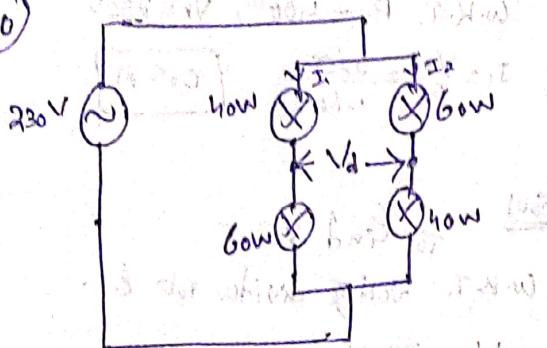Sol

W.K.T.

$$V_f = 230V$$

find branch curr individual

$$I_1 = I_2 = \frac{V}{R} = \frac{230}{2204.16} = 0.104348$$

Voltage drop across 60W

$$\sqrt{(60W)} = \frac{881.66}{2204.16} \times 230 = 91.922$$

(Ans.)

$$\begin{aligned} \sqrt{(60W)} &= I \times R_{(60W)} \\ &= 0.104 \times 881.66 = 91.999 \end{aligned}$$

$$\approx 92$$

$$\sqrt{(40W)} = I_1 \times R_{(40W)}$$

$$= 0.104348 \times 1322.5$$

= 138.

$$\sqrt{d} = \sqrt{(60W)} - \sqrt{(40W)}$$

$$= 138 - 92$$

$$\sqrt{d} = 46V$$