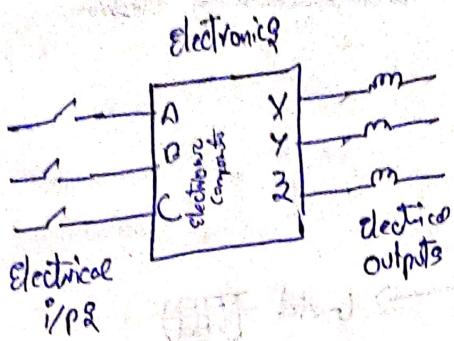


Electronics



mathematics - mathematics



physics → physical

mechanics
optics

$$x \xrightarrow{f_n} y$$

$$y = f_n(x)$$


Journey

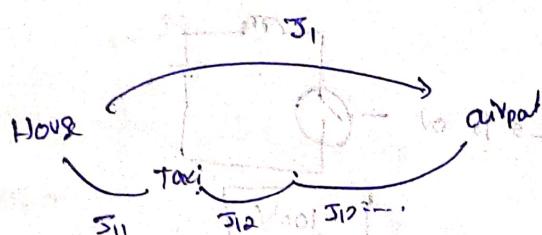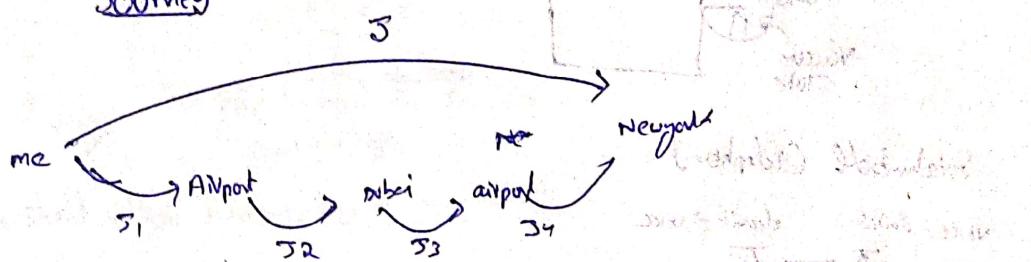

Control


(electro) manual

Automatic (electronic)

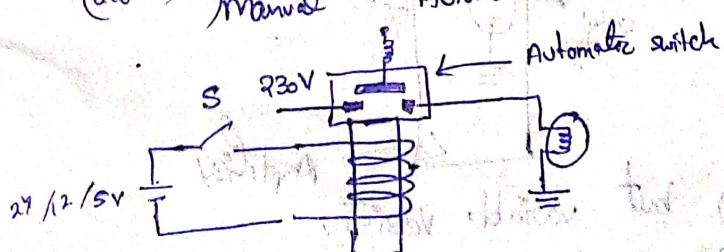


Distributors

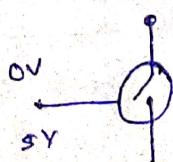- slow
- contact damage
- wear
- tear
- spring



Electron \rightarrow Electron


electron carrying electric

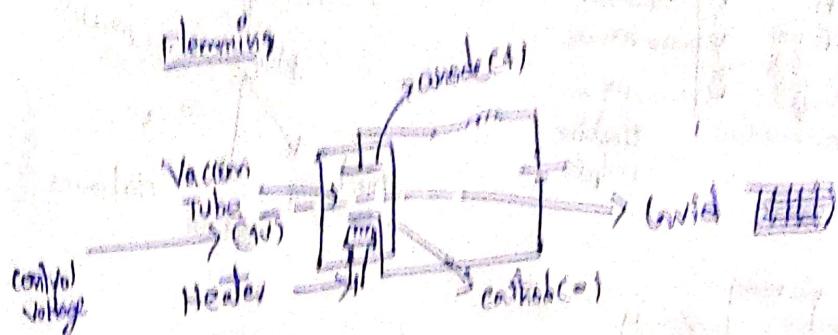



Led Zeppelin each electronic compn is TV tube






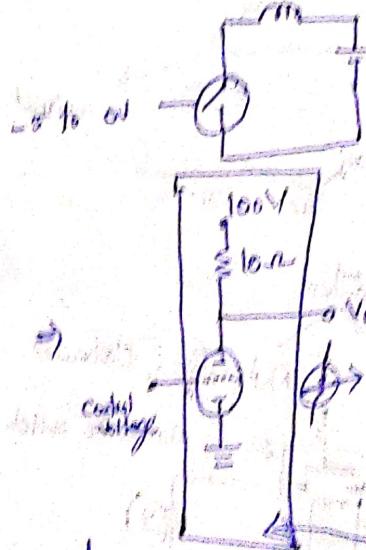
(Waldemarbeck Creaphone)
voice - input direct - voice
 $R_1 = 10^5$



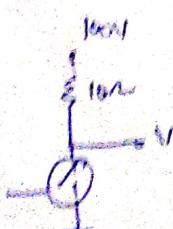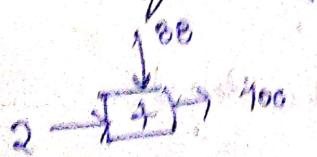
Amplifier is nothing but variable voltage amplifier



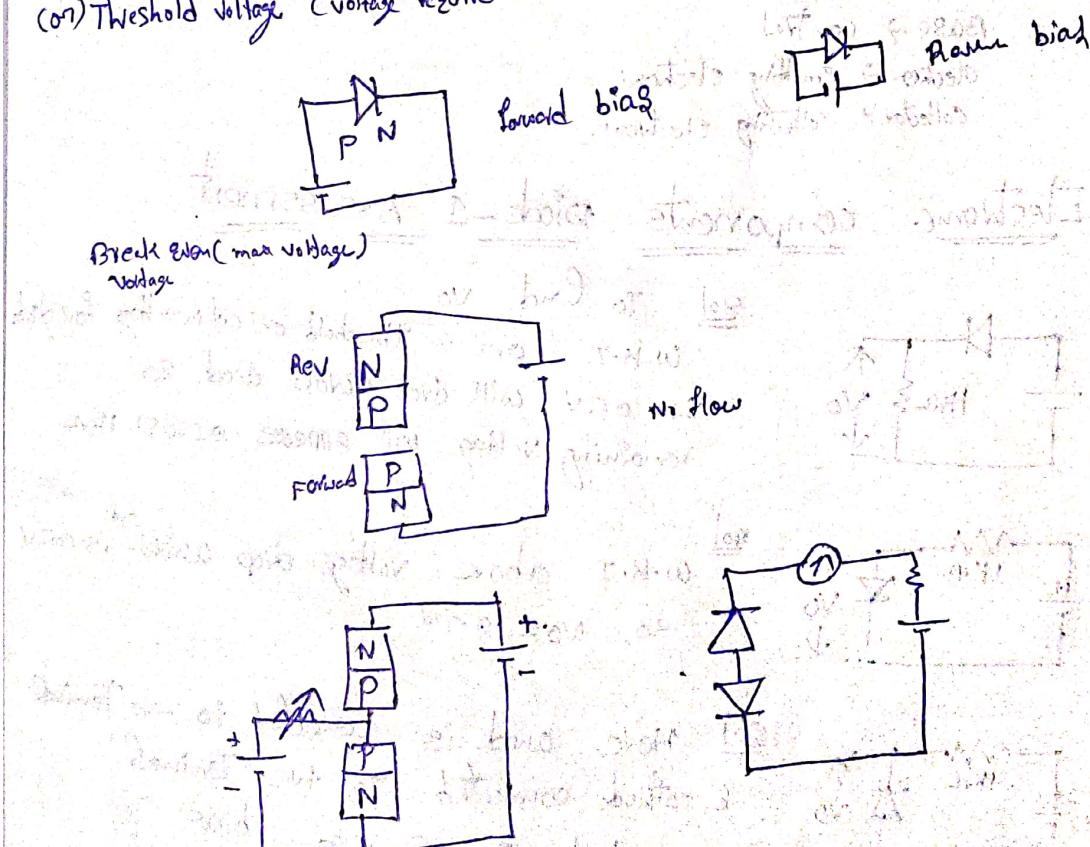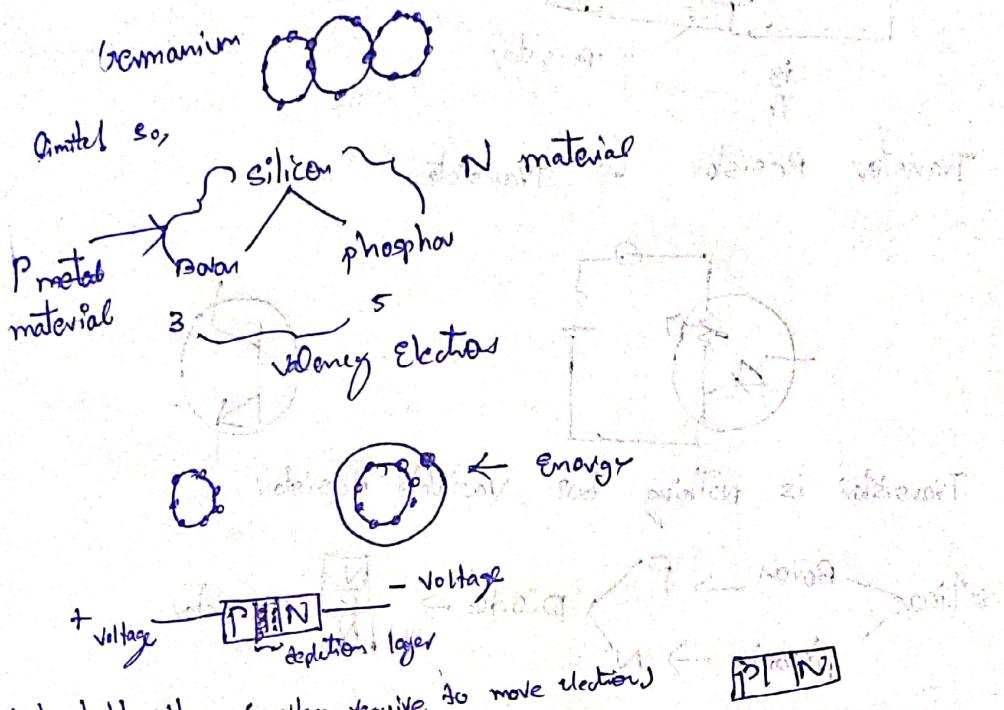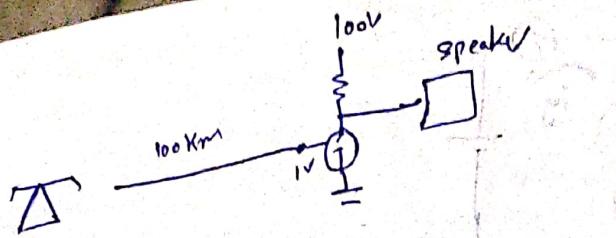

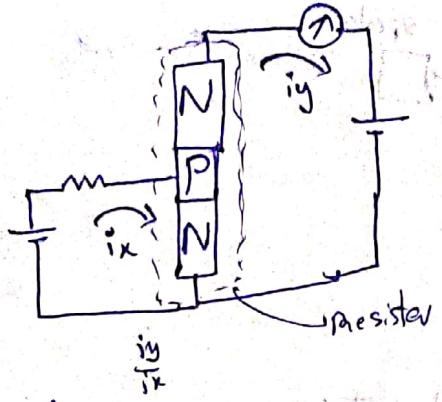

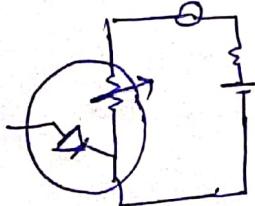Transistor Resistor \rightarrow Transistor




Transistor is nothing but Variable Resistor

silicon $\xrightarrow{\text{Boron}} \text{P}$ Diode \rightarrow  Transistor
 $\xrightarrow{\text{phospho}} \text{N}$

Base \rightarrow control
 electron \rightarrow emitting electron
 collector \rightarrow collecting electron


Electronic components Diode - I Assessment

①

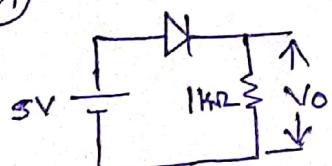


Sol To find V_o
 W.K.T. $0.7V$ is threshold or cut-in voltage for diode
 So, $0.7V$ will drop across diode so
 Remaining voltage will appear across $1k\Omega$

②








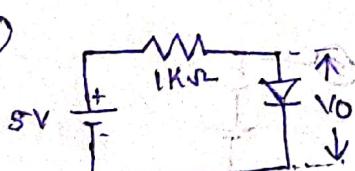


Sol W.K.T above, voltage drop across diode is $0.7V$
 So, $V_o = 0.7V$


③

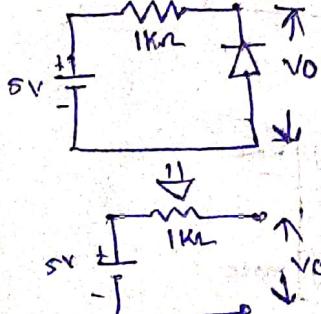

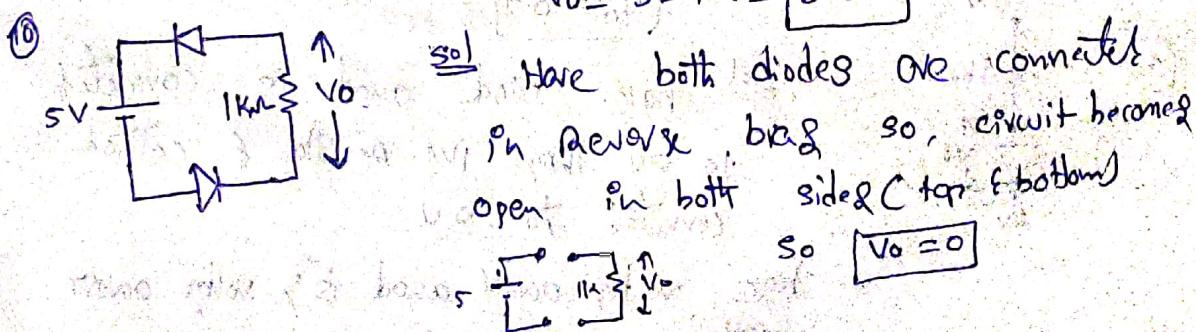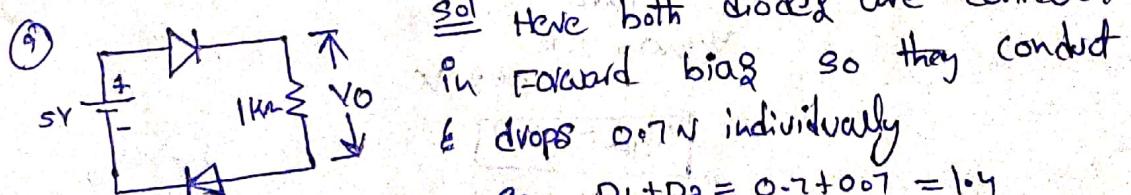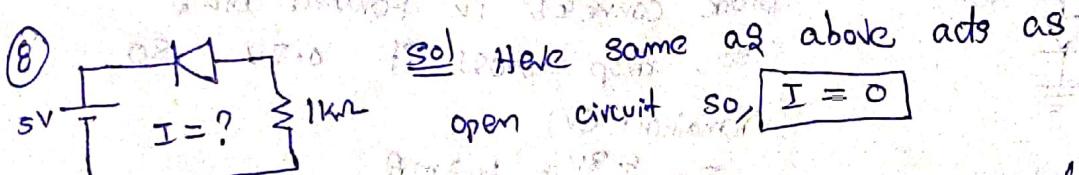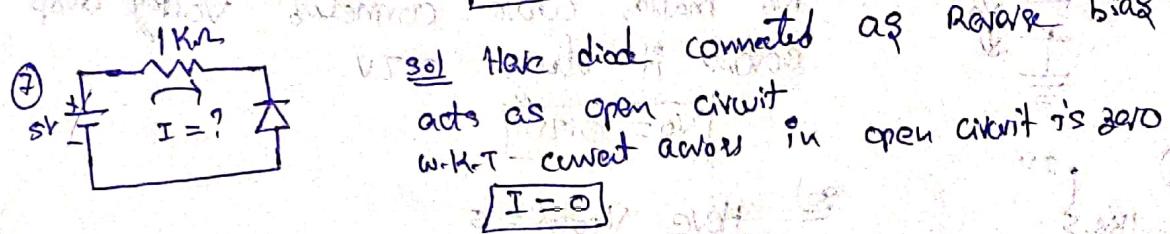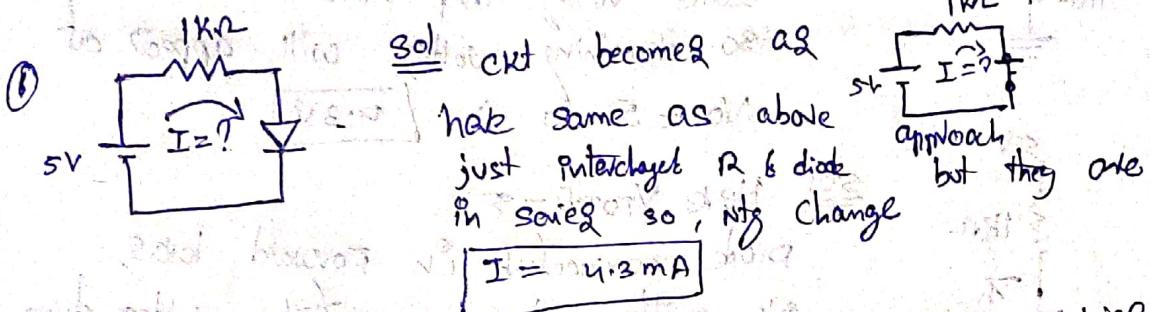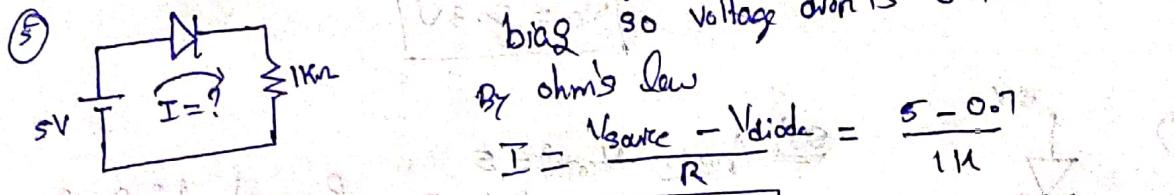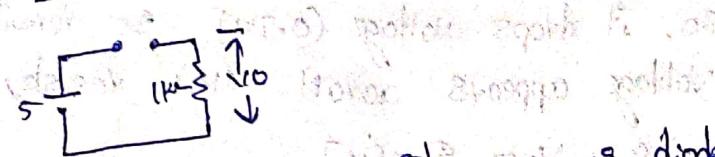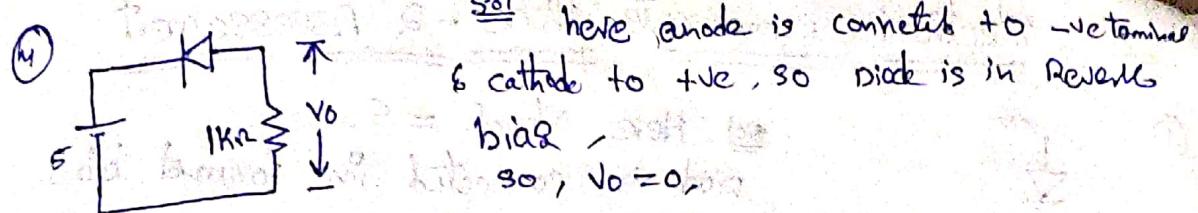Sol Here anode is connected to +ve Terminal & cathode connected to -ve Terminal
 So, diode in Reverse bias
 So, it acts as open circuit
 we know that across two terminals 5V will appear (due to open circ)



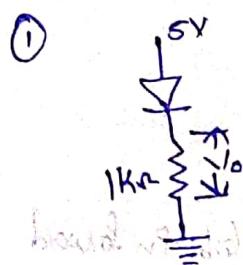
Electronic components diode - 2 Assessment




Sol Here $V_{\text{Total}} = 5$,
diode is connected in forward bias
so, it drops voltage (0.7V) so remaining
voltage appears across 1kΩ resistor

$$V_o = 5 - 0.7$$

$$\boxed{V_o = 4.3 \text{ V}}$$

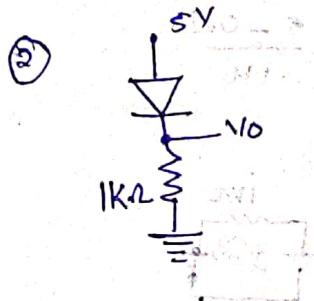


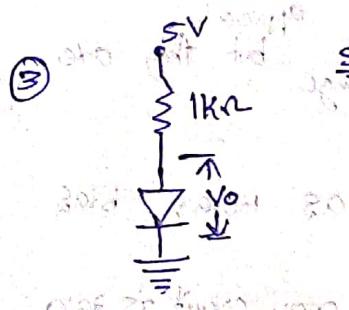Sol Here $V_{\text{Total}} = 5$
diode connected in forward bias so,
same voltage drop across it 0.7V
so remaining voltage will appear at
 $V_o = 5 - 0.7 \Rightarrow \boxed{4.3 \text{ V}}$



Sol Here $V_{\text{Total}} = 5$
diode connected in forward bias,
no matter where connected voltage drop
across it always 0.7V

$$\boxed{V_o = 0.7 \text{ V}}$$

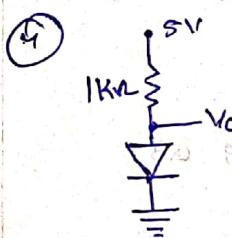

Sol Here $V_{\text{Total}} = 5$
diode connected in forward bias
so, drop across it 0.7V so
 $I = \frac{4.3 \text{ V}}{1 \text{ k}\Omega} = 4.3 \text{ mA}$


$$V_{(1 \text{ k}\Omega)} = I \cdot R$$

$$\boxed{V_{(1 \text{ k}\Omega)} = 4.3 \text{ V}}$$

$$V_o = 5 - V_{(1 \text{ k}\Omega)}$$

$$= 5 - 4.3$$

$$\boxed{V_o = 0.7}$$

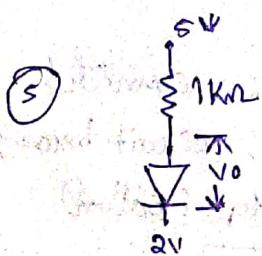

Sol here diode anode is connected
to 5V then 1kΩ resistor & cathode
connected to 2V

here voltage across anode is > voltage across
cathode

Diode is forward biased

so voltage drop is always $0.7V$ only

⑥ so Here diode is connected in forward bias ($V_{Cathode} > V_{Anode}$)

$$so, V_o = 2 + V_{diode}$$

$$= 2 + 0.7 \\ V_o = 2.7$$

(Q1)

By KVL

$$5V - (I \times 1k\Omega) - V_{diode} - 2V = 0.$$

$$w.k.t. 10 \\ V_{diode} = 0.7$$

$$5 - (I \times 1k\Omega) - 0.7 - 2 = 0$$

$$5 - (I \times 1k\Omega) = 2.7 \quad (Q1) \quad 5 - 2.7 - (I \times 1k\Omega) = 0$$

$$\Rightarrow 2.3 - (I \times 1k\Omega) = 0$$


$$2.3 = I \times 1k\Omega$$

$$I = \frac{2.3}{1k\Omega} = 2.3mA$$

$$V_{IR} = IR \\ = 2.3mA \times 1k\Omega \\ = 2.3V$$

$$V_o = 5 - V_{IR}$$

$$V_o = 2.7V$$

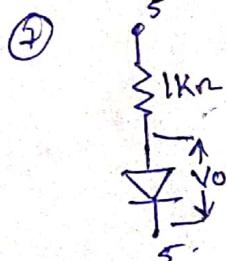

⑦ so Here we can see that anode is connected to 5V through 1kΩ resistor & cathode is connected to 5V directly

so $V_{Cathode} \neq V_{Anode}$ so voltage drop

so diode is ~~forward biased~~ so

across it is $2V$

$$V_o = 0$$


ideal case




so Here again diode connected in reverse bias

so circuit is open but we measure


V_o above diode upto that 5V mark

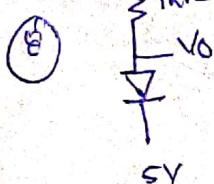(due to open circ^(short circuit) no current will flow so there will be zero across 1kΩ resistor)



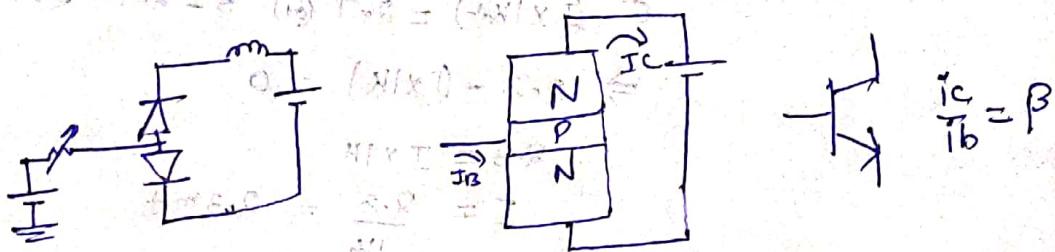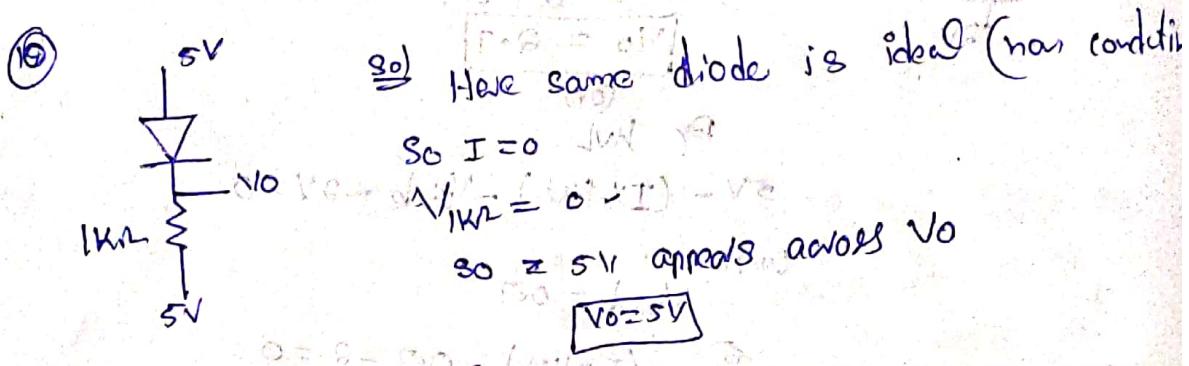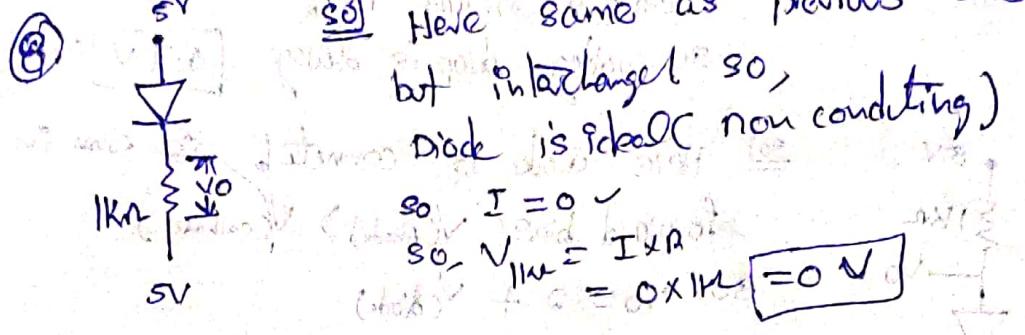


β - amplification factor

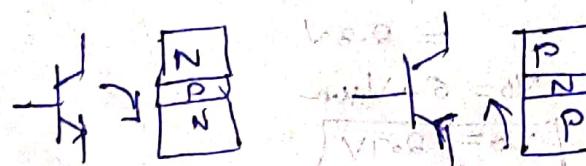

$$V_b - V_{BE} \downarrow$$

$$i_B = \frac{V_b - V_{BE}}{R_b}$$


$$\beta = 10$$

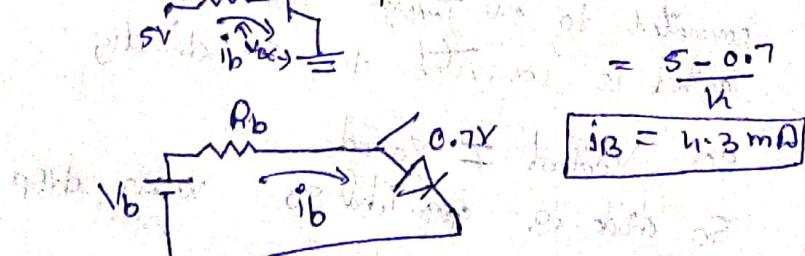

$$② I_C = \beta I_B = 10 \times 0.7 \text{ mA} \Rightarrow 7 \text{ mA}$$

$$③ V_C = I_C \times R_C \Rightarrow 7 \text{ mA} \times 1k\Omega \Rightarrow 7 \text{ V}$$

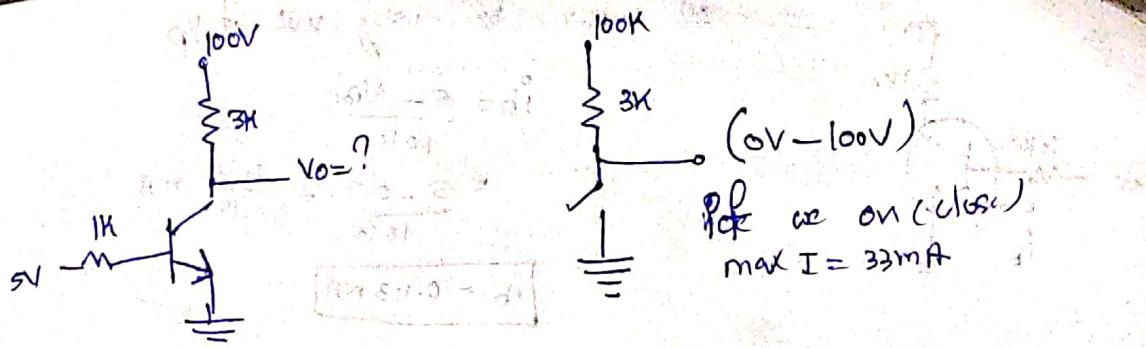
$$④ V_o = 100 - V_C \\ = 100 - 7 \text{ V}$$




off
1
saturation
if $i_c > i_{cmax}$
then $i_c = i_{cmax}$

cut-off
saturation
switch
→ Gate → digital electronics
logic functions
Variable resistor
amplifier → analog electronics
Amplifiers, voltage regulators

Transistor characteristics

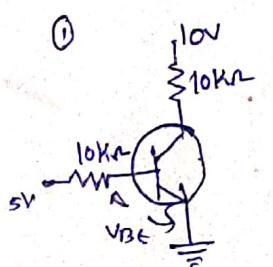

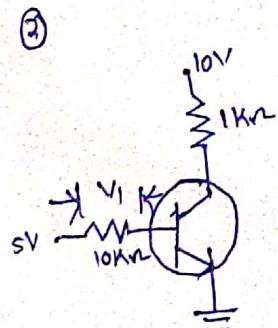① apply V_{BL} at np side
 $V_{BE} = 0.7$ V for silicon
that $V_{BE} = 0.7$ directly








② apply V_{BL} at np side


$$5V - V_I - V_{BE} = 0$$

$$5V - V_I - 0.7 = 0$$

$$V_I = 5V - 0.7$$

$$\boxed{V_I = 4.3V}$$

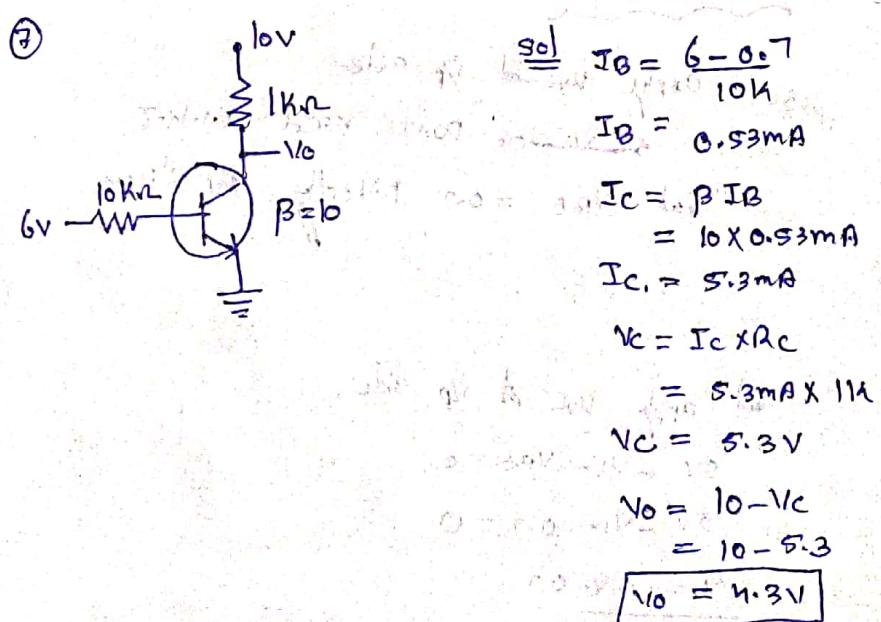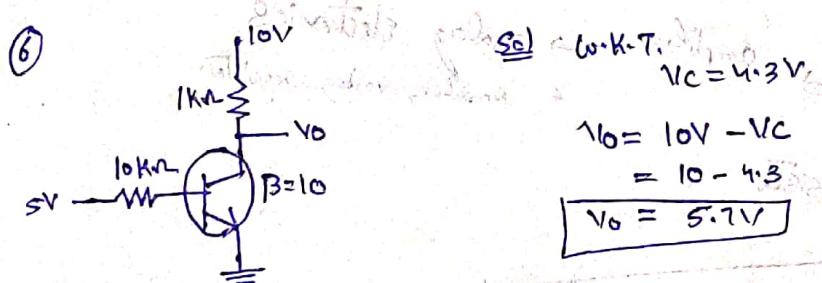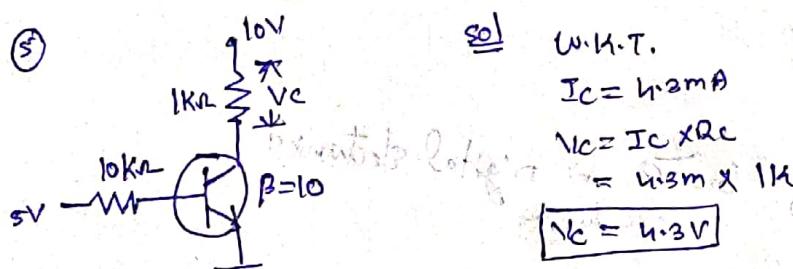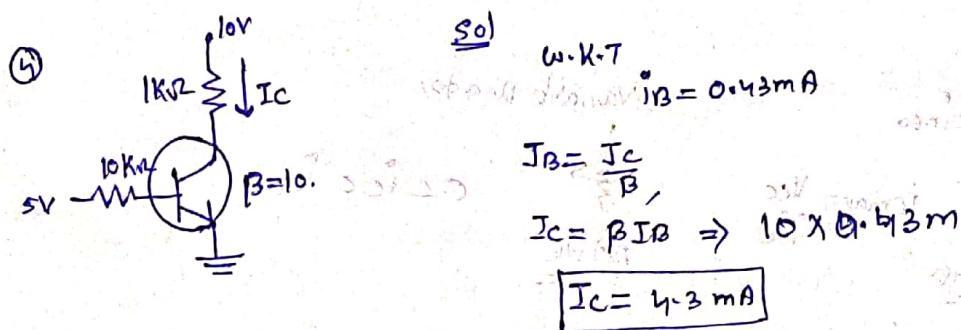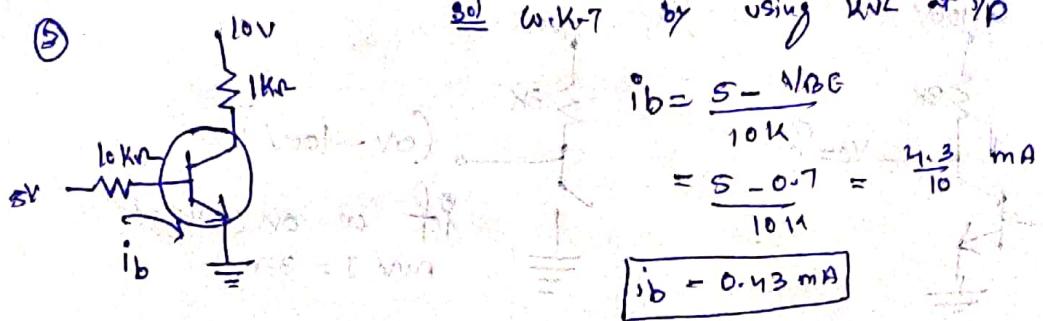


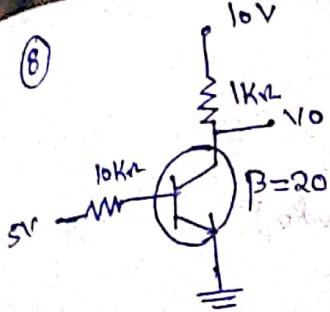

$$I_B = \frac{5 - 0.7}{10k} = 0.43mA$$


$$\begin{aligned} I_C &= \beta I_B \\ &= 20 \times 0.43mA \\ I_C &= 8.6mA \end{aligned}$$
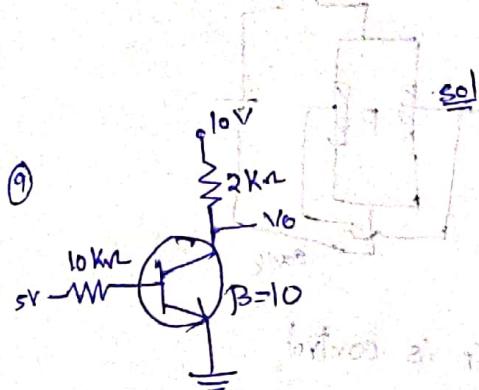
$$\begin{aligned} V_C &= I_C \times R_C \\ &= 8.6mA \times 1k \\ V_C &= 8.6V \\ V_O &= 10 - V_C \Rightarrow 10 - 8.6 \\ V_O &= 1.4V \end{aligned}$$



$$\begin{aligned} I_B &= 0.43mA \\ I_C &= \beta I_B \\ &= 10 \times 0.43mA \\ I_C &= 4.3mA \end{aligned}$$
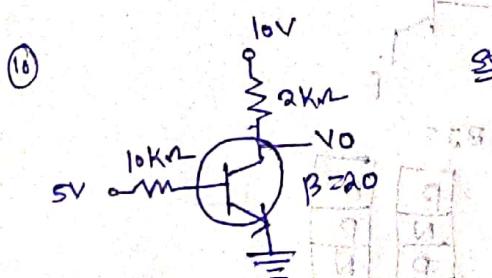
$$\begin{aligned} V_C &= I_C \times R_C \Rightarrow 4.3mA \times 2k \\ V_C &\rightarrow 8.6V \\ V_O &= 10 - 8.6 \\ V_O &= 1.4V \end{aligned}$$



$$I_B = \frac{5 - 0.7}{10k} = 0.43mA$$

$$\begin{aligned} I_C &= \beta I_B \\ &= 20 \times 0.43mA \\ I_C &= 8.6mA \\ V_C &= I_C \times R_C \\ &= 8.6mA \times 2k \\ V_C &= 17.2 \\ V_O &= V_{CC} - V_C \\ &= 10 - 17.2 \\ V_O &= -7.2 \end{aligned}$$

here -ve sign indicated it is in saturation generally in active
 ~~V_o~~ should V_O should be in b/w
 (to V_{CC}) only.

because $I_C \gg I_{Cmax}$
 So it drives into saturation mode

$$I_{Cmax} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10 - 0.2}{2k} = 4.9mA$$

$$I_{Cmax} = \frac{9.8V}{2k\Omega} = 4.9mA$$

$$\therefore I_C \gg I_{Cmax} \quad \text{this condition makes } I_C = I_{Cmax}$$

$$V_C = I_C \times R_C \Rightarrow 4.9mA \times 2k$$

$$V_C = 9.8V \quad V_O = V_{CC} - V_C \Rightarrow 10 - 9.8 = 0.2V$$



Voltage controlled device

current controlled device



(Bipolar junction)

$$S_i + B = P$$



$$S_i + P = N$$

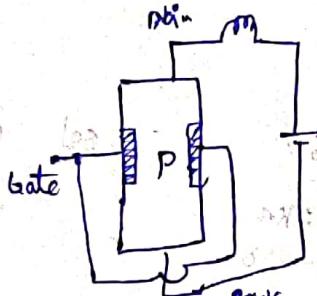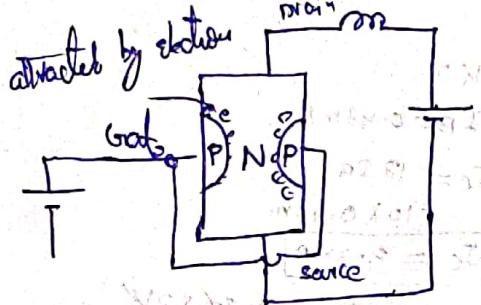

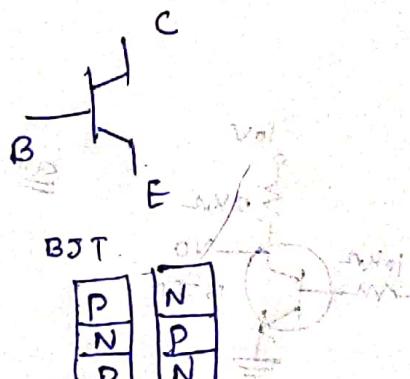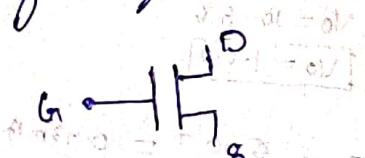By applying voltage at gate I_D is control




Field effect Transistor

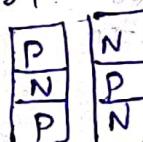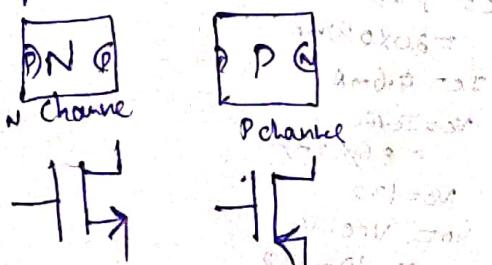

BJT faster than FET (due to capacitance charging and discharge time more)

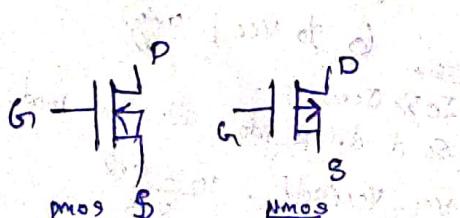perfect insulator we use (SiO_2) in MOSFET



metal oxide semiconductor field effect
Transistor