
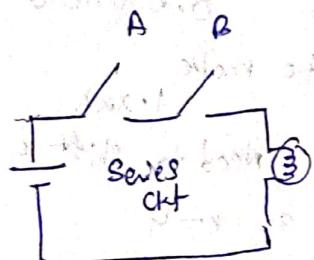



# Digital Electronics

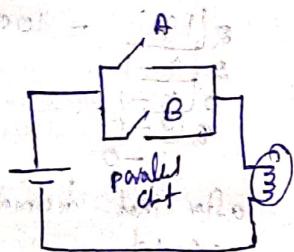


if A AND B are ON, then bulb is ON



if A OR B is ON, bulb is ON

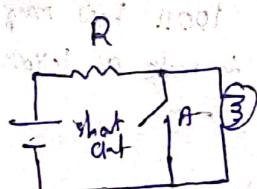

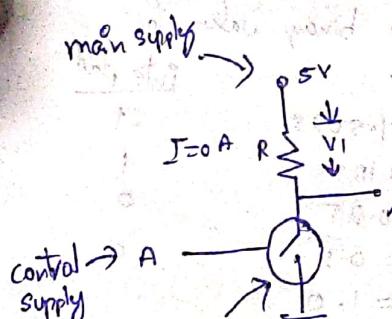if A is ON, B is OFF  
if A is OFF B is ON



if  $A=0, Y=1$


$A=1, Y=0$

$$Y = V - V_1 \quad (V_1 = 0 \text{ V})$$

$$= 5 - 0$$

$$Y = 5$$


Transistor  
as switch

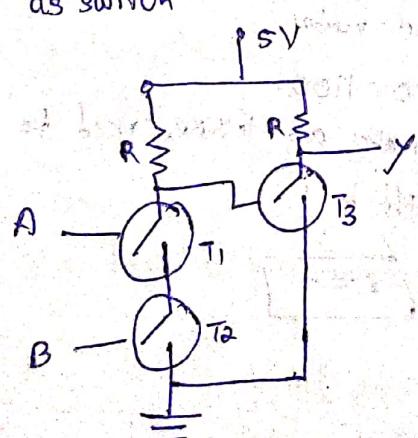




if  $A=B=0$ , then  $T_3$  will get 5V


then it turns ON  $y=0$ . (bcz it is GND)

A	B	Y
0	0	0
5V	0	0
0	5V	0
5V	5V	5V

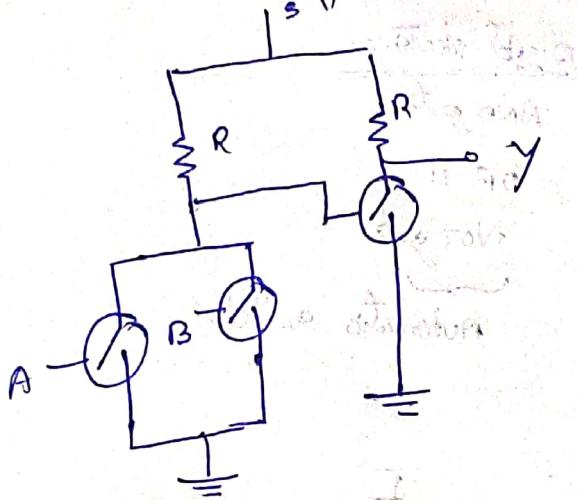

A	B	Y
SV	0	SV
0	SV	SV
0	0	0V
SV	SV	SV

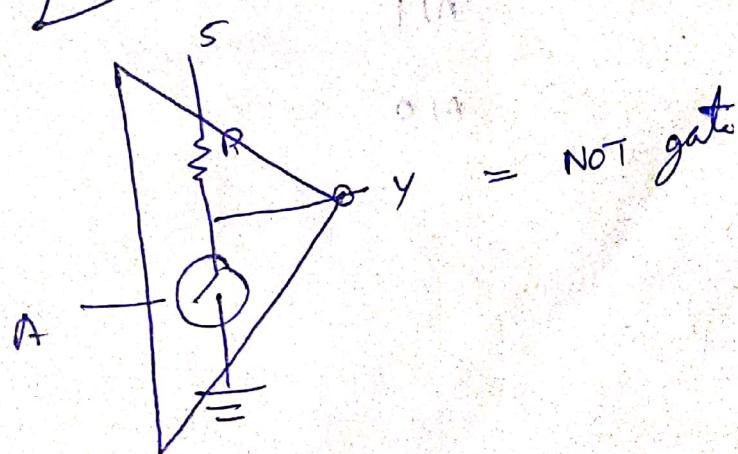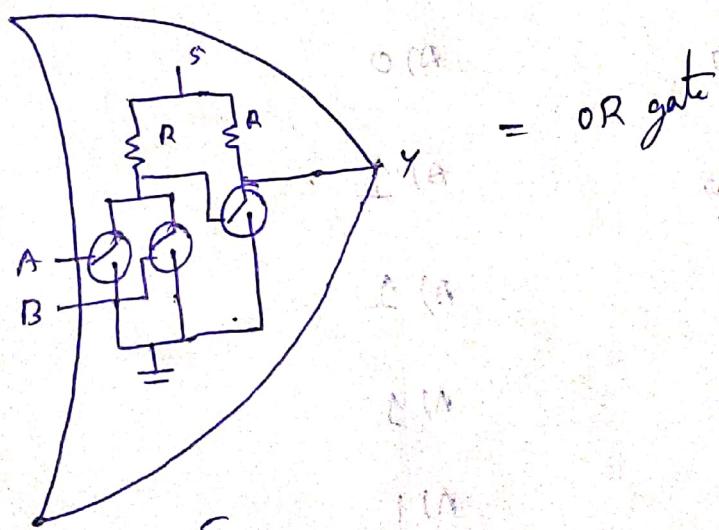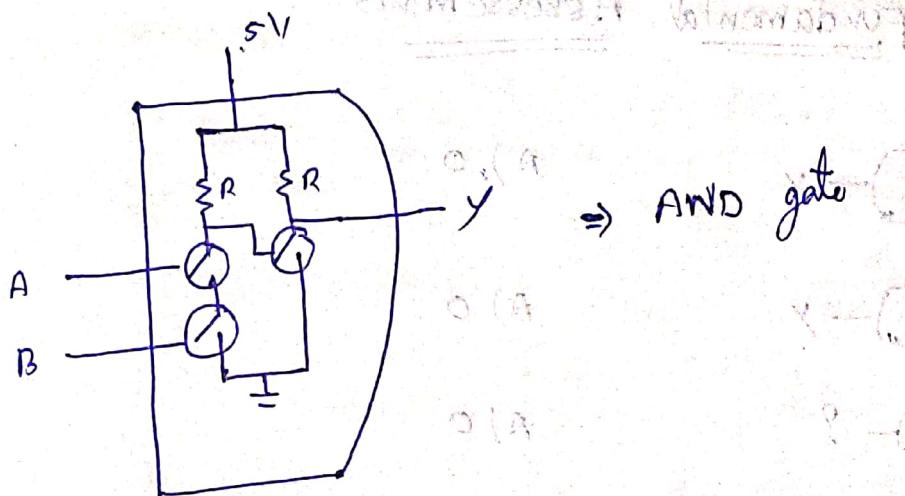

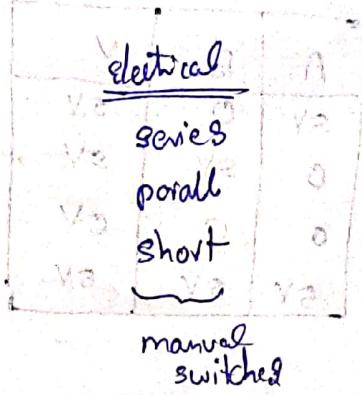

Digital electronics

AND gate

OR II

NOT gate

automatic switch


## Fundamental Assessments

①




A) 0

⑤

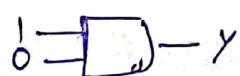


A) 0

③

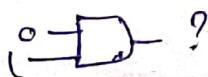

A) 0

⑥

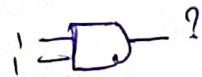

A) 1

⑤



A) 0

⑩



A) 1

⑦




A) 1

⑧




A) 1

⑨

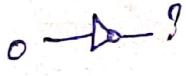


A) 1



⑩

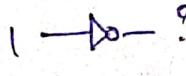


A) 0

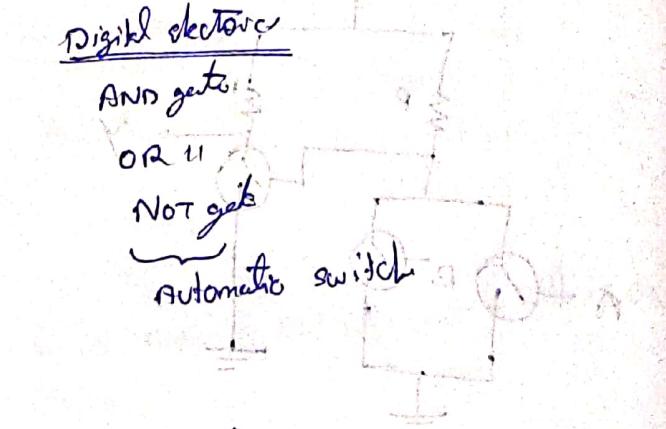



## Assessments

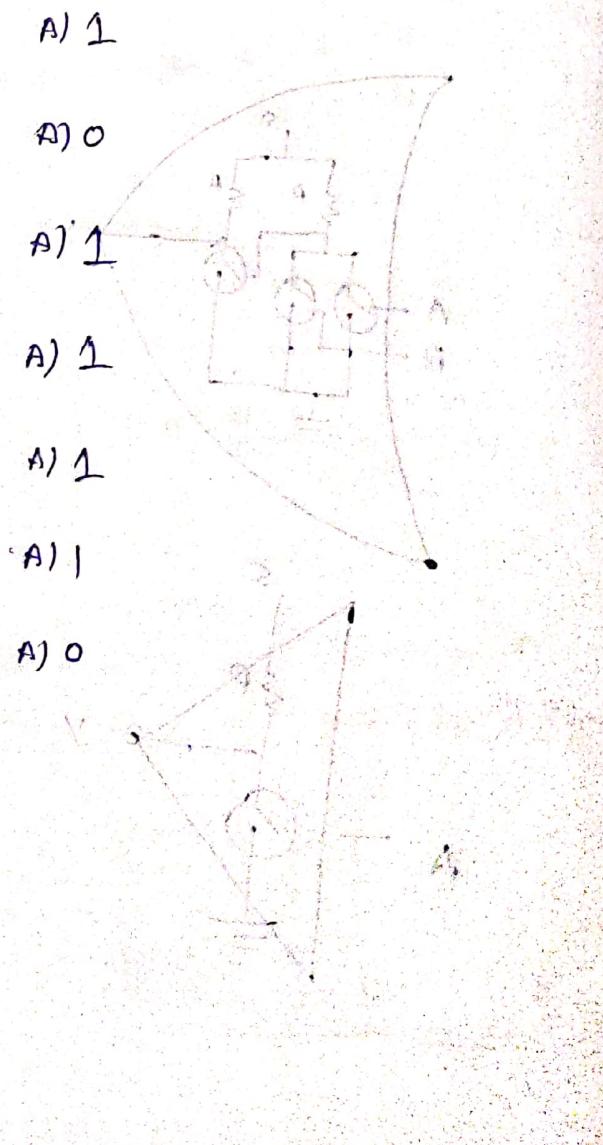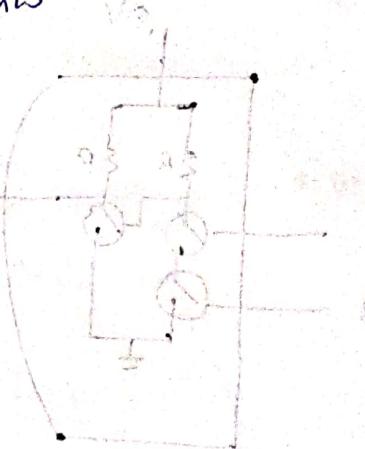



## Combinational logic

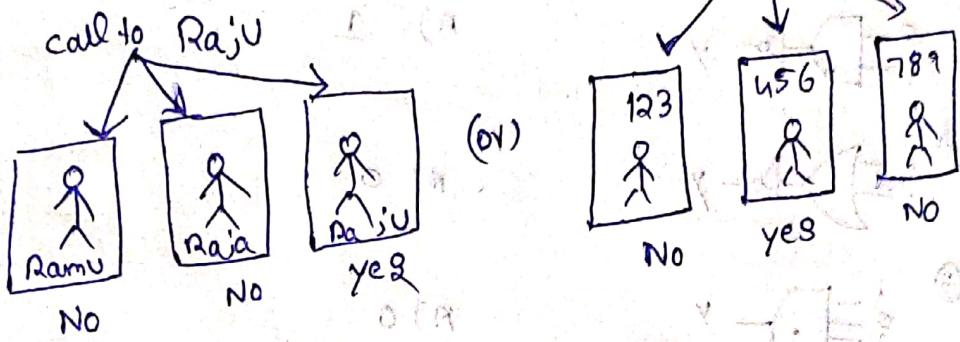

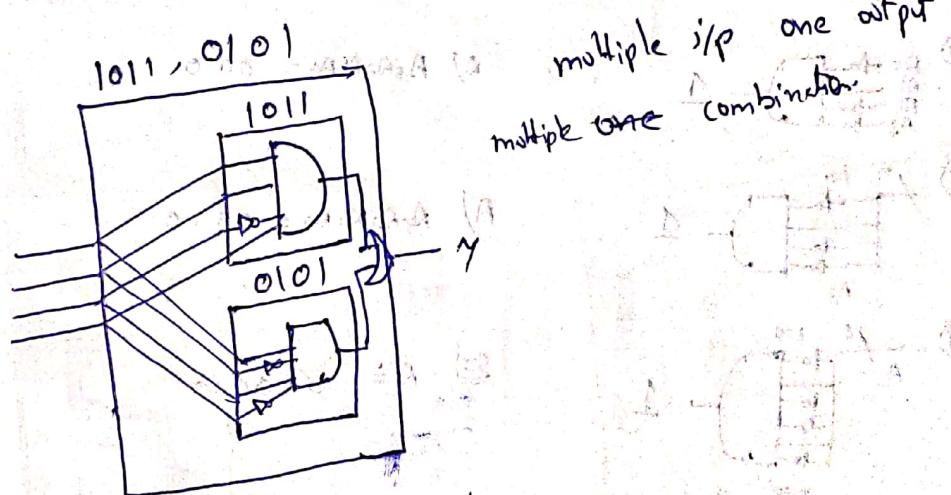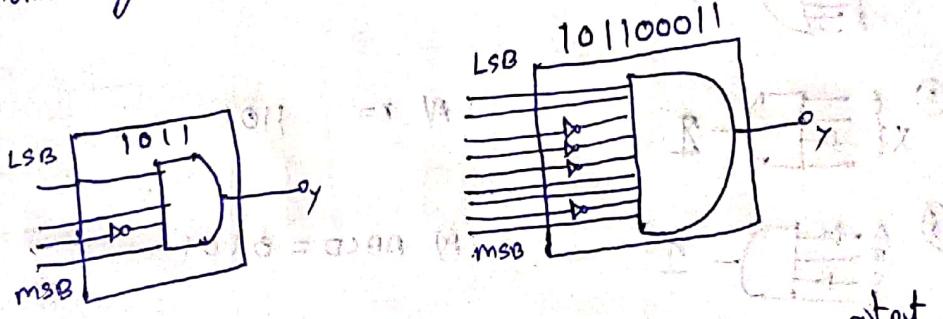combinational logic Nothing but Binary name



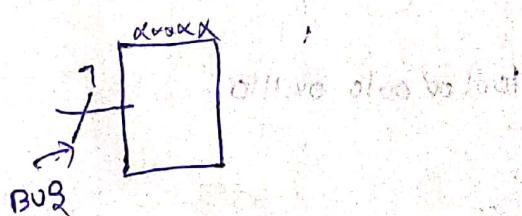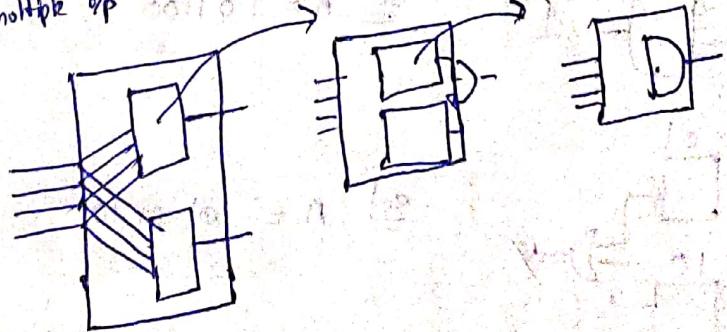multiple i/p multiple o/p multiple combinations




# combinational logic assessment




A) 1




A) 0

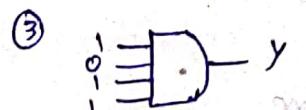


A) 0

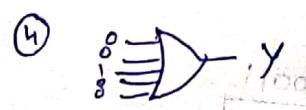


A) 1

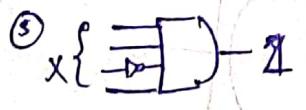


A)  $x = 1101$

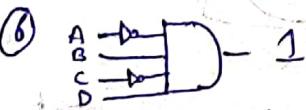


A)  $ABCD = 0101$

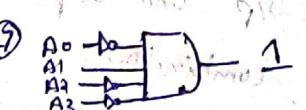


A)  $A_3A_2A_1A_0 = 0010$

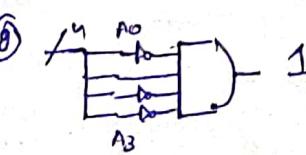


A)  $A_3A_2A_1A_0 = 0010$

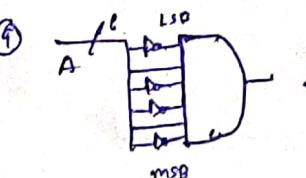


sol A = 010010

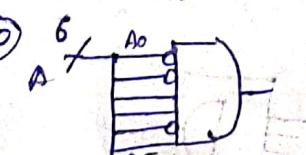


sol A = 101100

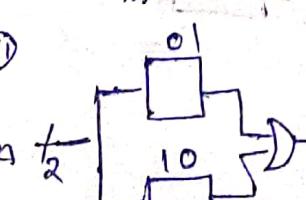


sol A = 01 or 10

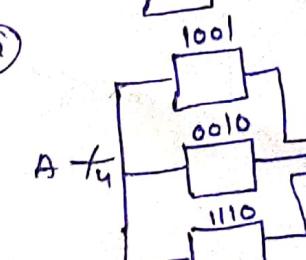



sol 1001 or 0010 or 1110

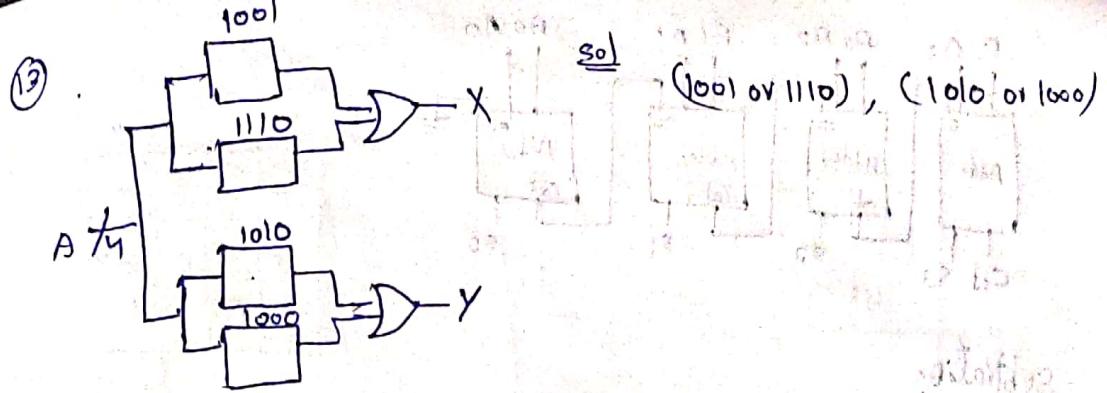

## Application of logic

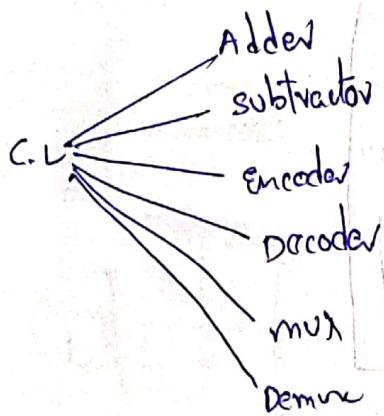

### Adder

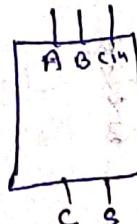
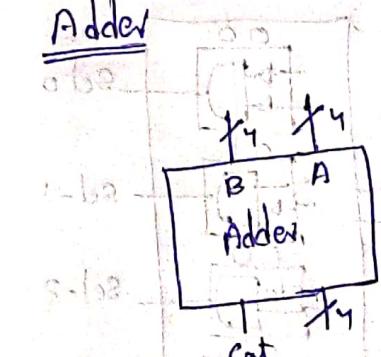



c <sub>in</sub>	B	A	Cout	S
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

sum truth table


c <sub>in</sub>	A	S
0	0	1
0	1	0
1	0	0
1	1	1

c <sub>in</sub>	B	A	C <sub>out</sub>
0	1	1	1
1	0	1	1
1	1	0	1
1	1	1	0

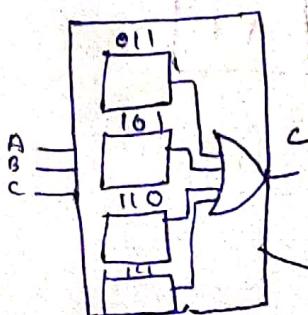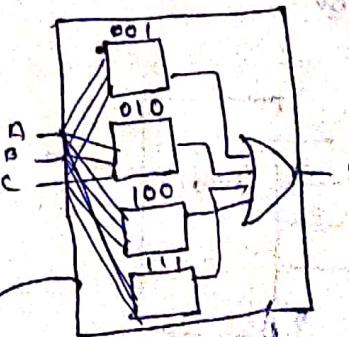


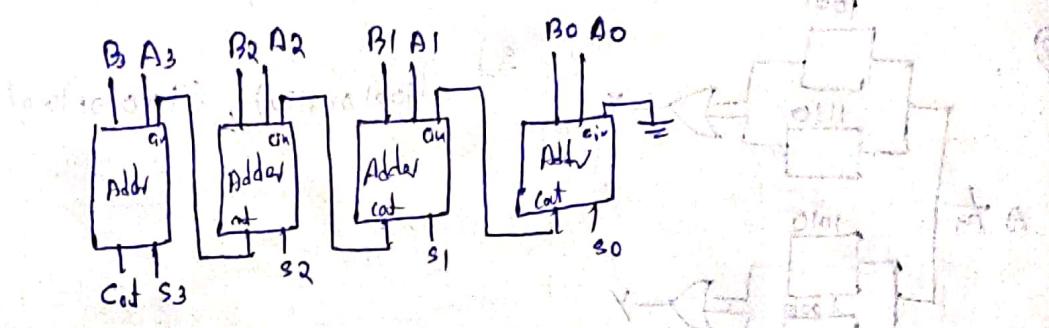


### Subtraction

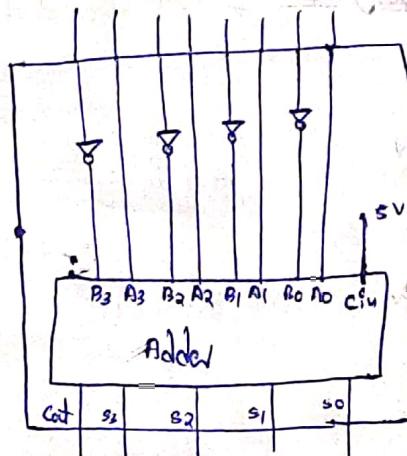

### Decoder





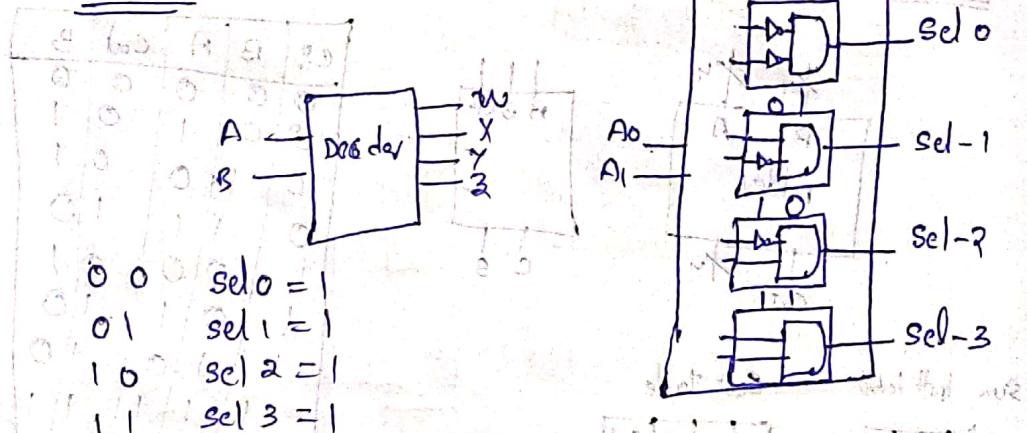


### Encoder

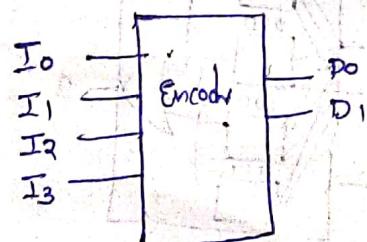


$J_3 J_2 J_1 J_0$	$I_0$	$P_1 P_0$
0 0 0 1	0 0	0 0
0 0 1 0	0 1	0 1
0 1 0 0	1 0	1 0
1 0 0 0	1 1	1 1

# Combinational logic assessment

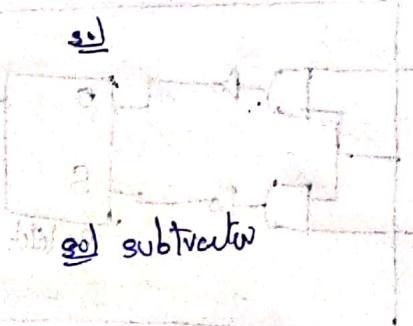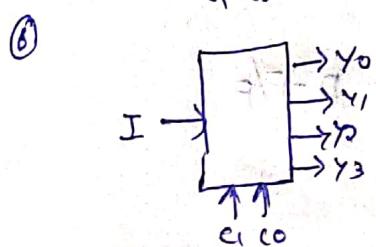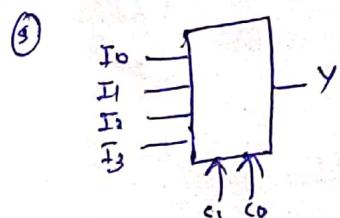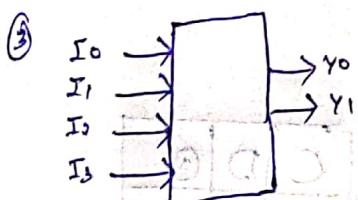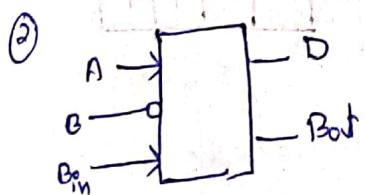


a) Encoder

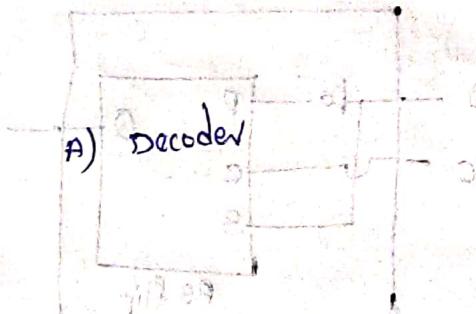


A) Decoder

a) MUX

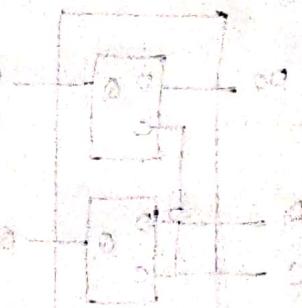

Sequential logic

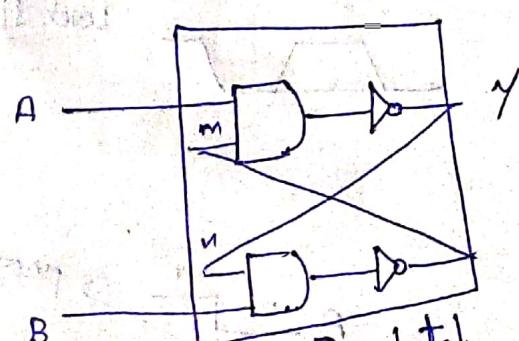


start with zero

1) 11 {after} 10 then  $y = 0$

2) 11 {after} 01 then  $y = 1$


R S Qn

A	B	Y
1	0	0
1	1	0
0	1	1
1	1	1


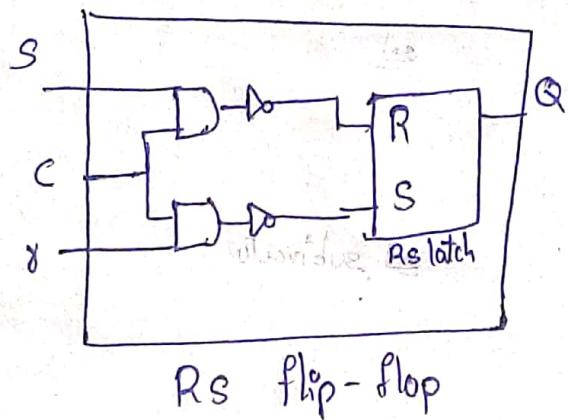


C	R	S	Q
0	X	X	Q <sub>n-1</sub>
1	1	0	0
1	0	1	1


D-Flip flop

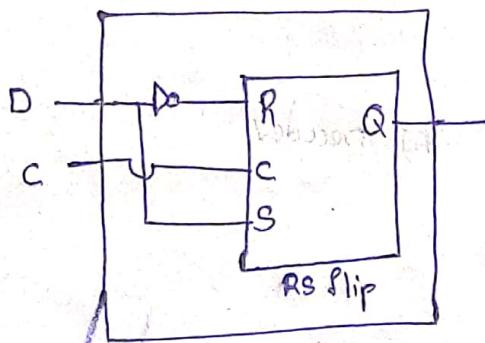


C	D	Q
0	X	Q <sub>n-1</sub>
1	0	0
1	1	1

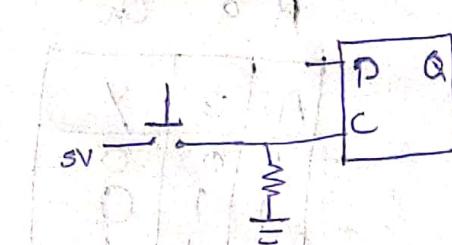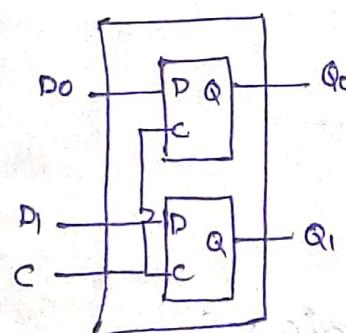


Level flip flop

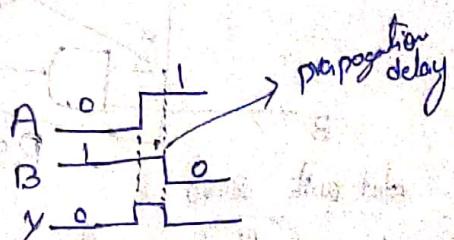


Edge triggered f/f

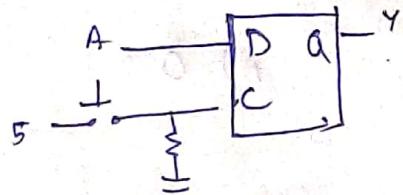


level trigger F/F

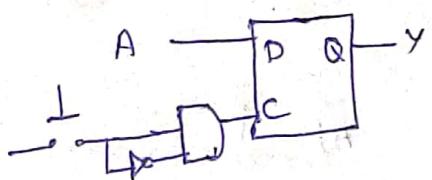


edge trigger F/F

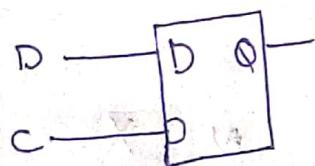


$\Rightarrow +ve$  level trigger

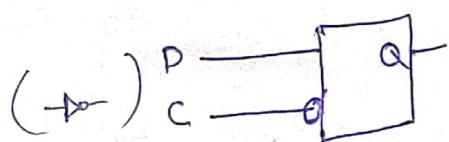

$\Rightarrow -ve$  level trigger

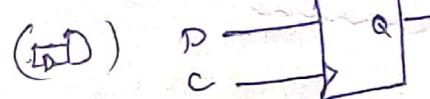


$\Rightarrow +ve$  trigger

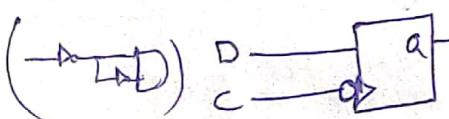

$\Rightarrow -ve$  trigger


sequential logic - assessment - 1

①

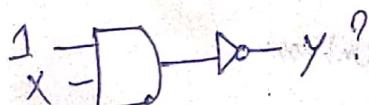

A) X

②

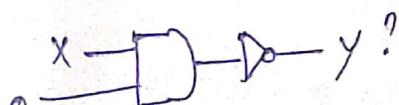


A) 1

③






A) 0






④

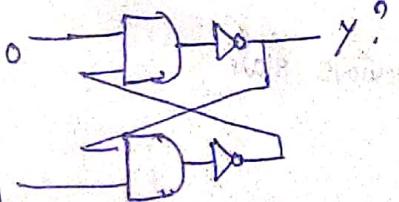


A) 1

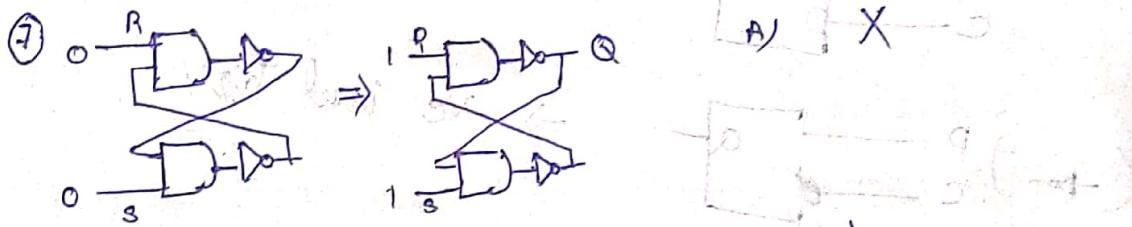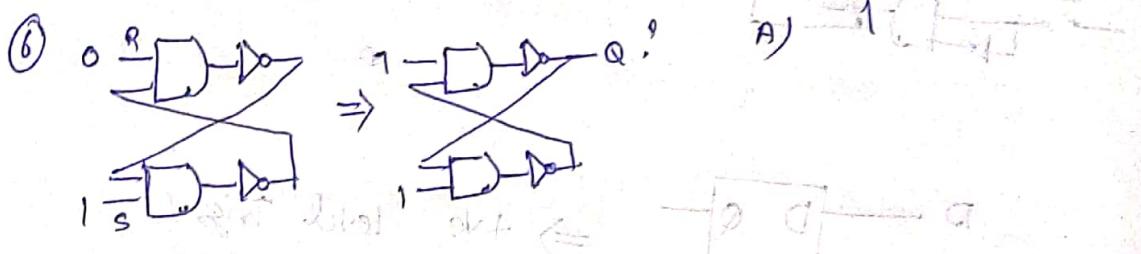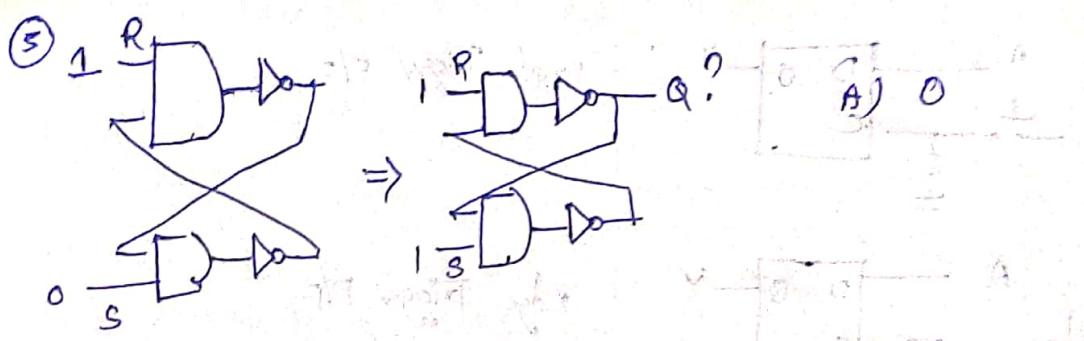


Sequential logic Q - Assessment

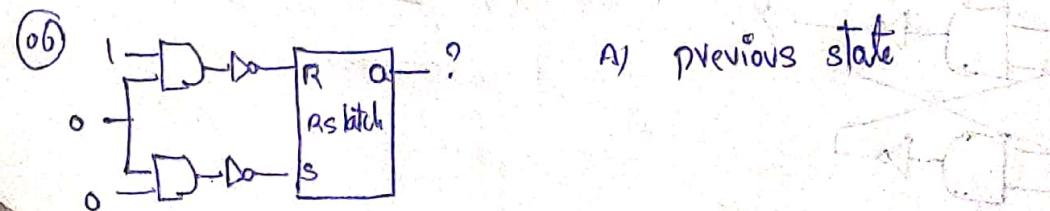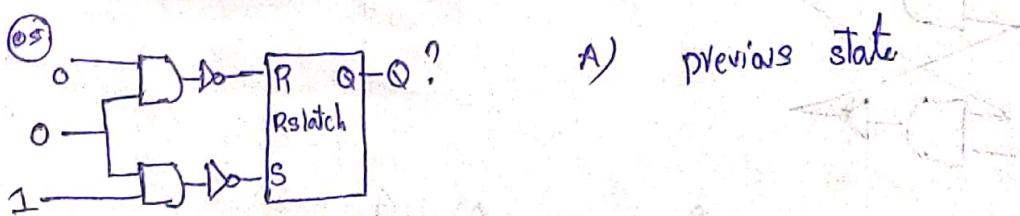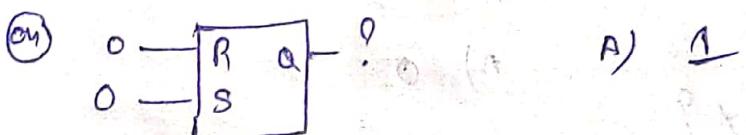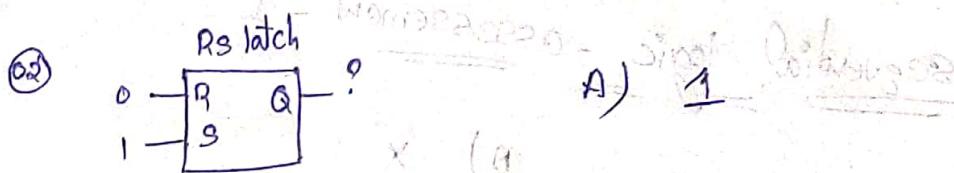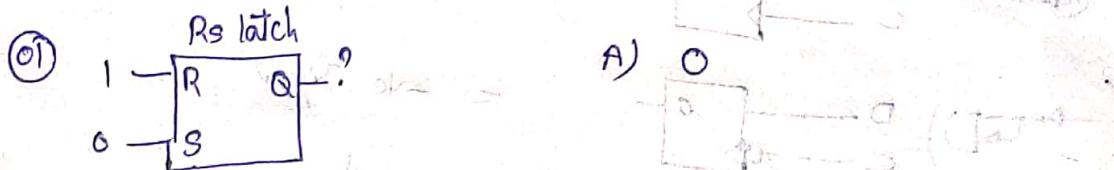


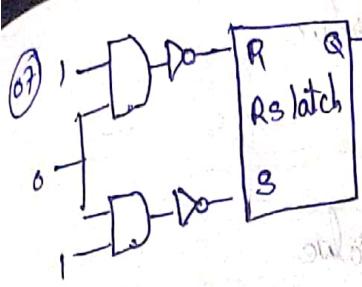


A) previous state

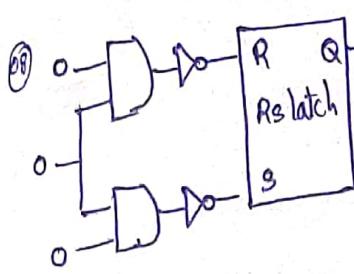


A) previous state

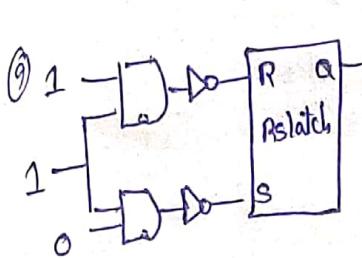


A) 1

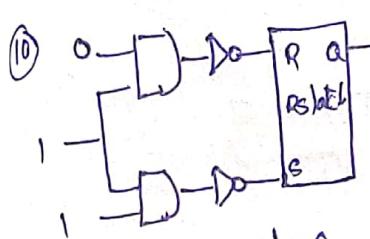


sequential logic problem part - 3

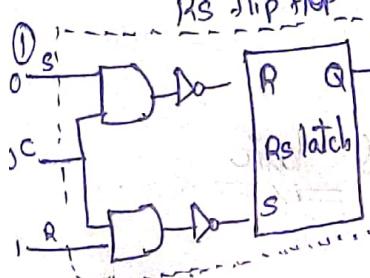


A) previous value

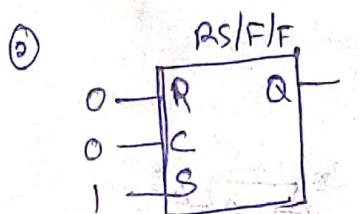







A) previous value

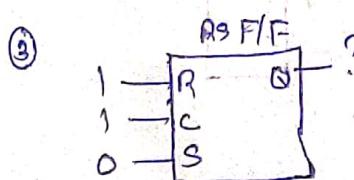

A) 0

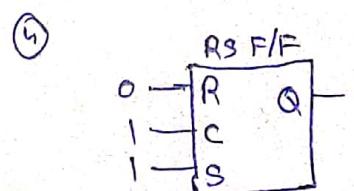


A) 1

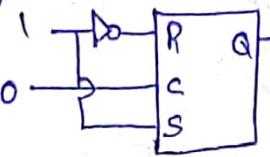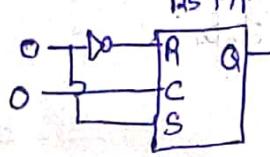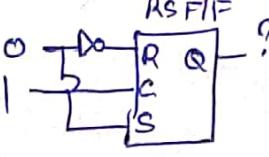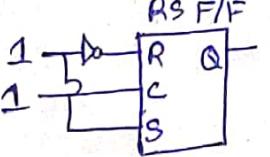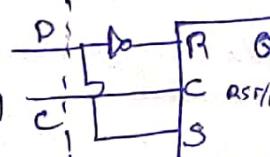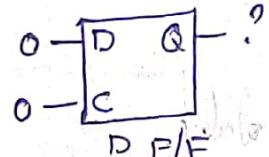- ⑤  A) previous value
- ⑥  A) previous value
- ⑦  A) zero
- ⑧  A) one
- ⑨  A) one  
D F/F
- ⑩  A) previous value  
D F/F





Applications of


sequential logic

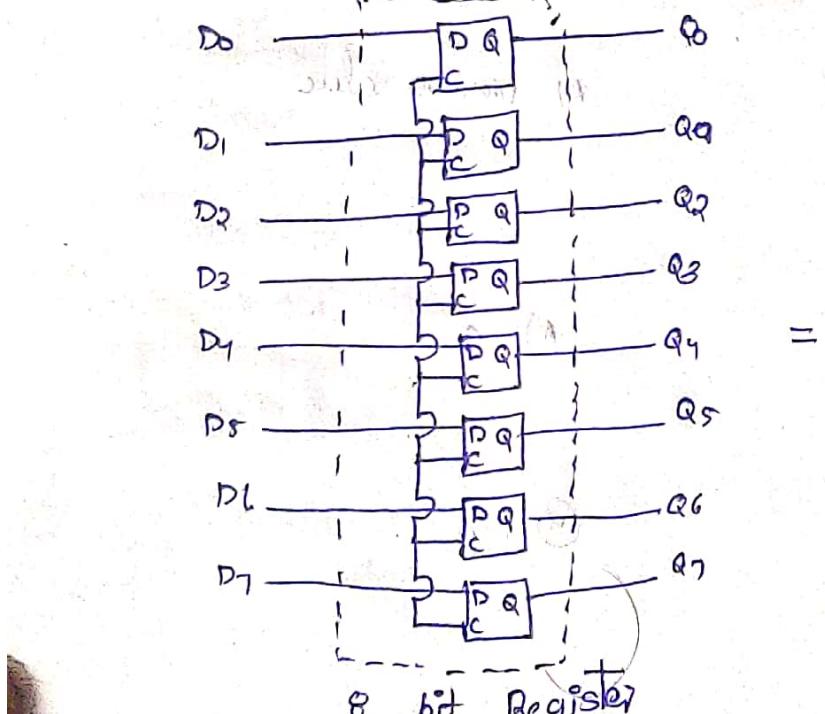


$$=$$



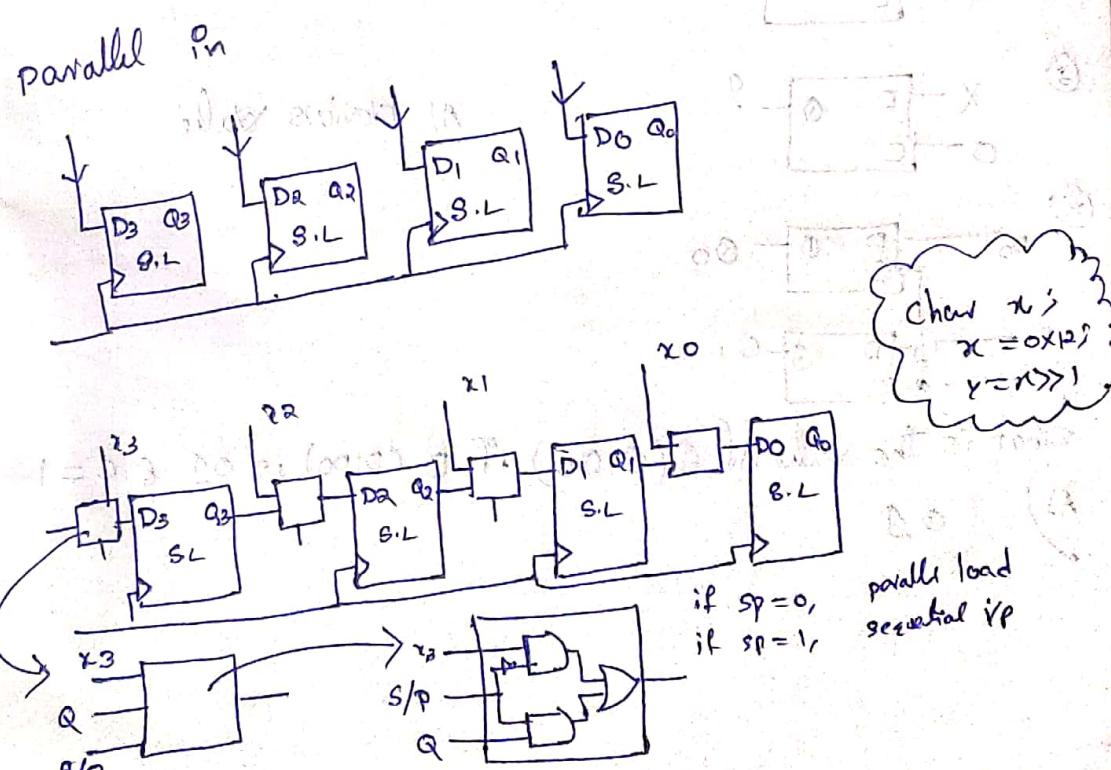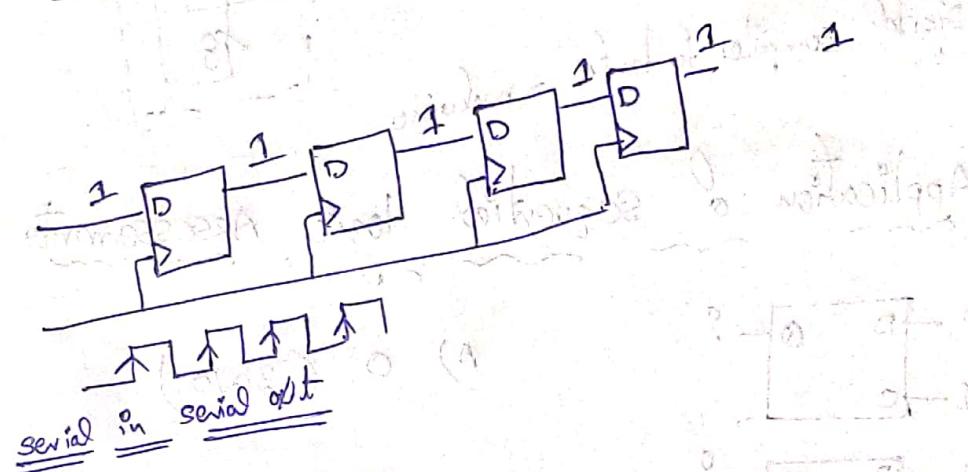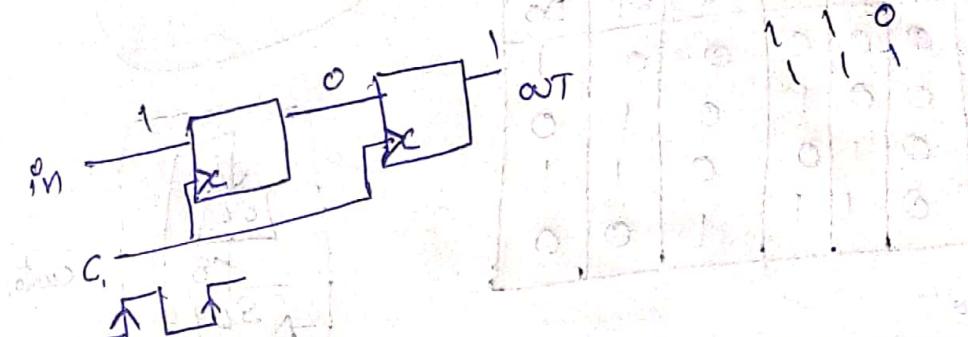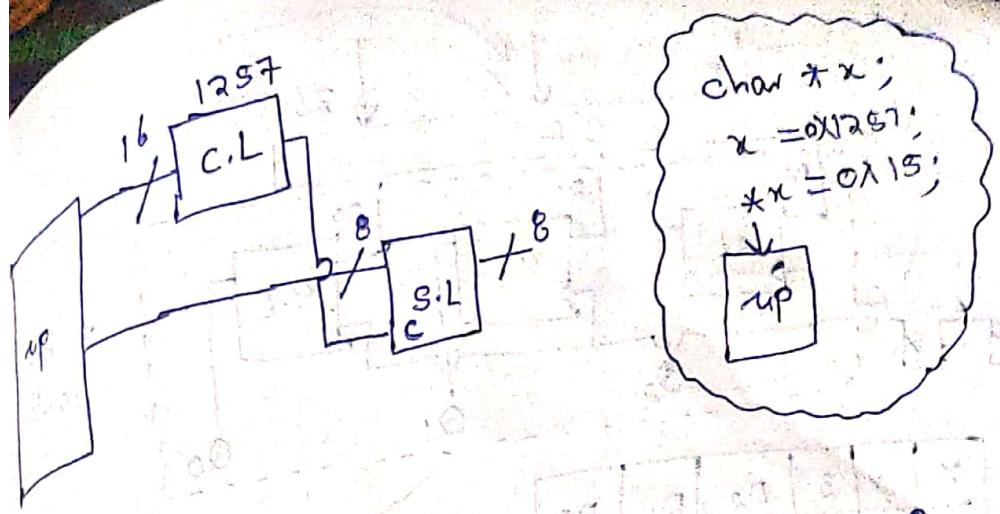

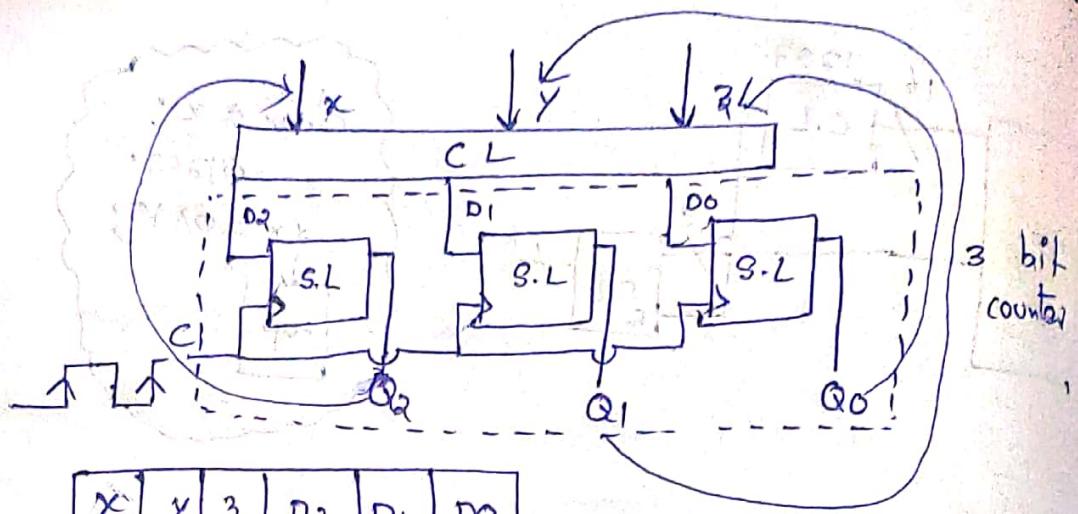


X	Y	z	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0

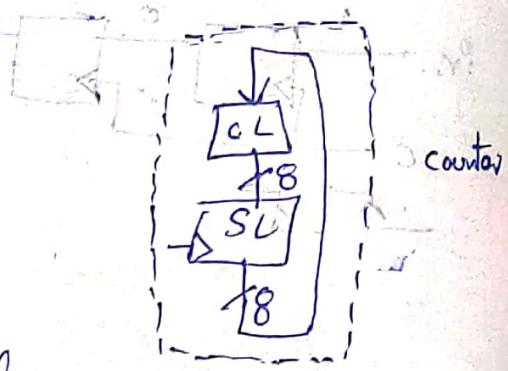


Best book

Digital computer fundamentals - including

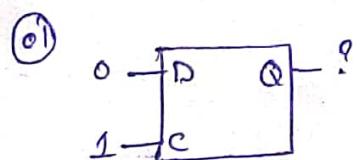
Application of sequential logic Assessments




A) 0 (Zero)

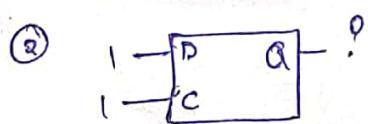

A) One

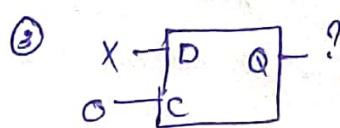


A) previous value

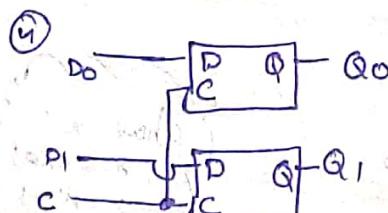

What is the value of Q1(Q1Q0), if D(D1D0) is 01 & C=1

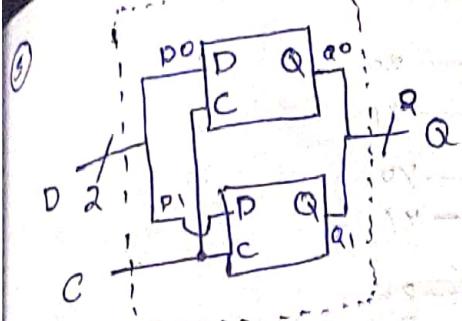
A) 01

what is the value of Q if  $D=10$   
 $c=1$



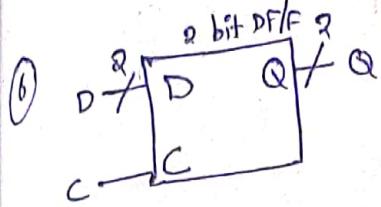
A) 10

what is the value of Q if  $D=10$   
 $c=1$



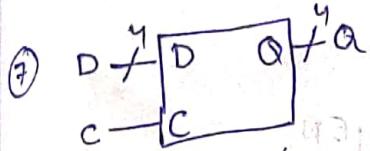
A) 10

what is the value of Q if  $D=1010$   
 $c=1$




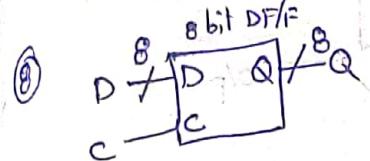A) 1010

what is the value of Q if  $D=10101010$   
 $c=1$




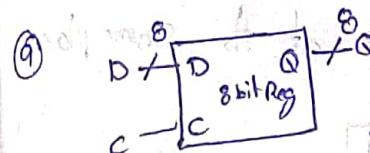what is the value of Q if  $D=10101010$   
 $c=0$




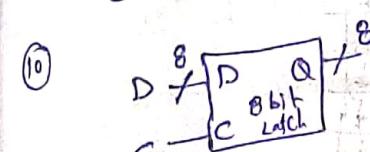
A) previous state

what is the value of Q if  $D=01010101$   
 $c=1$





A) 01010101

Tristate logic & its applications



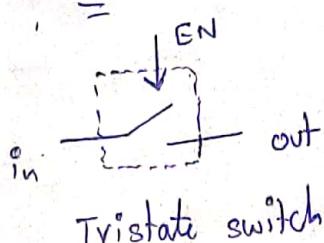
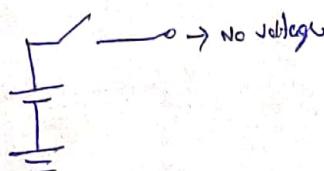



EN	IN	out
SV	SV	SV
SV	0V	0V
0V	X	No Voltage

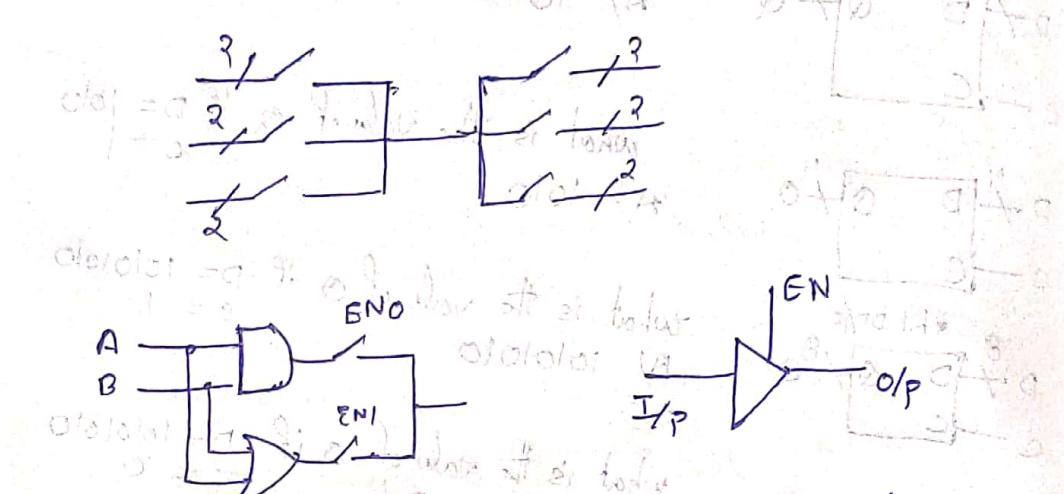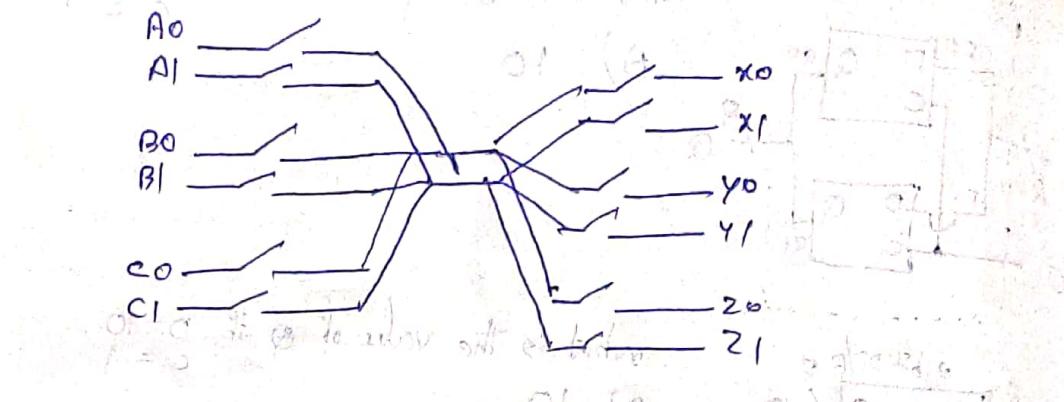

Note Never connect two ~~input~~ output of ~~to~~ same place

without Tristate

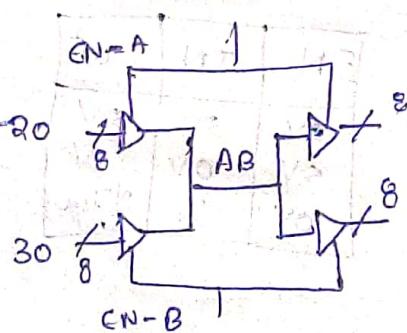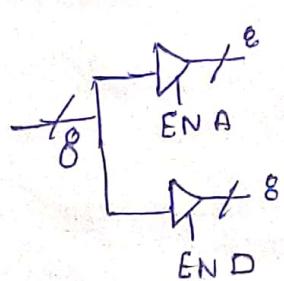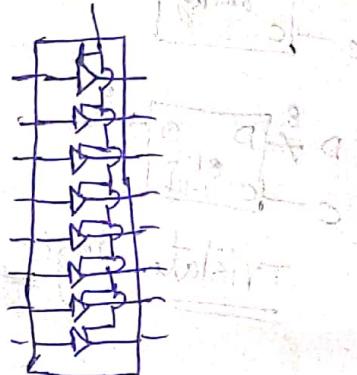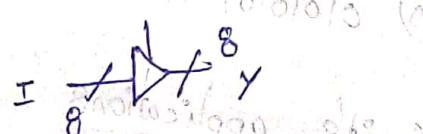

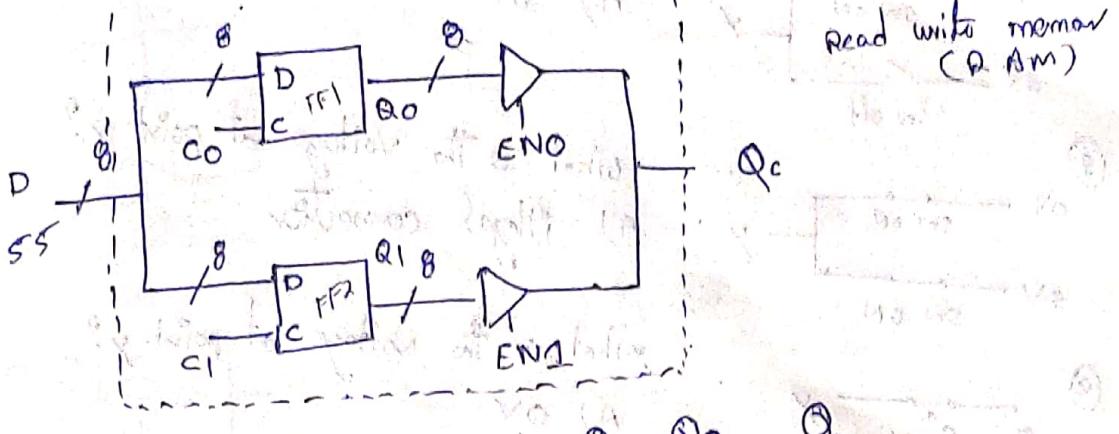


D	C0	C1	EN0	EN1	Q0	Q1	Qc
55	1	0	0	0	55	55	55
65	0	1	0	65	65	55	55
65	0	0	1	0	65	55	55
"	"	"	0	1	65	55	55

### Tristate logic assessment - 1

What is the voltage at point y?


1)

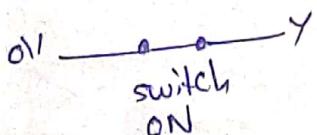

A) 0V

What is the voltage at point y?


2)

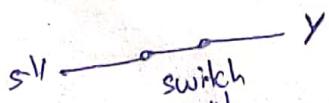

A) 5V

What is the voltage at point y?


3)

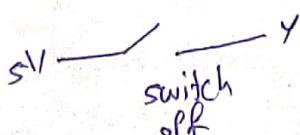

A) Floating voltage

What is the voltage at point y?


4)

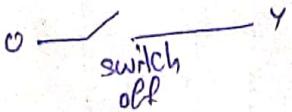

A) Floating voltage

What is the voltage at point y?


5)

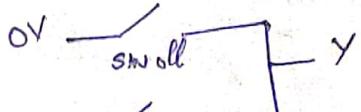

A) Floating voltage


What is the voltage at point y?


6)

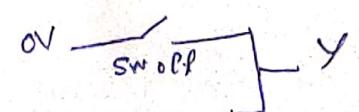

A) 5V


What is the voltage at point y?

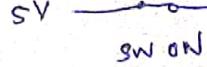

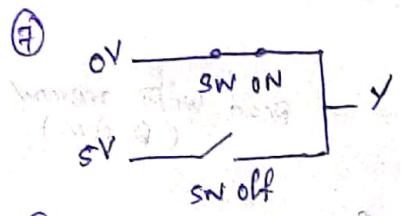


what is the voltage at point Y?

A) 0V

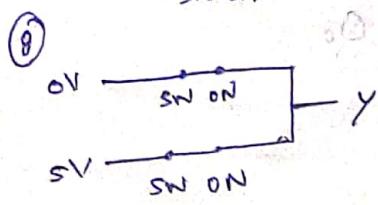

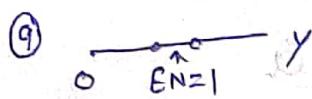what is the voltage at point Y?  
A) illegal connection




A) 0V




what is the voltage at point Y?  
A) floating voltage


## Tri-state logic assessment - 2

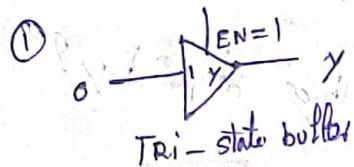

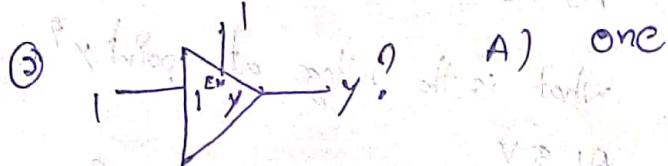
what is the logic value at point y?  
A) zero




A) one

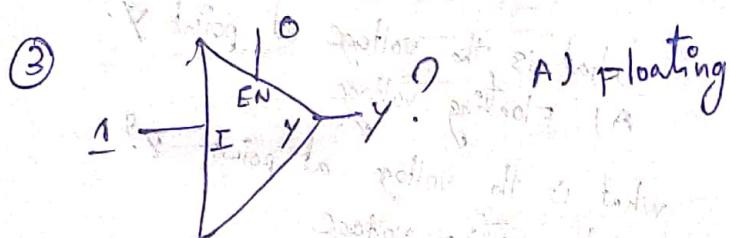


A) floating

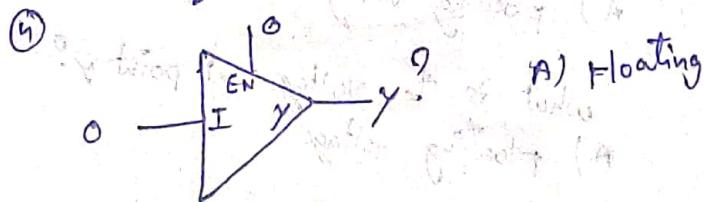




A) floating

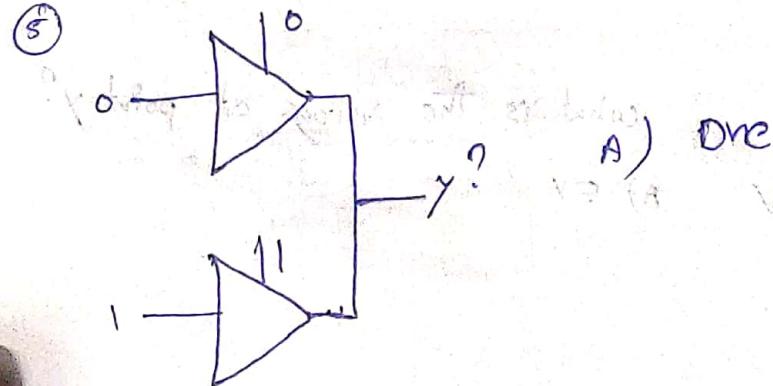

A) one

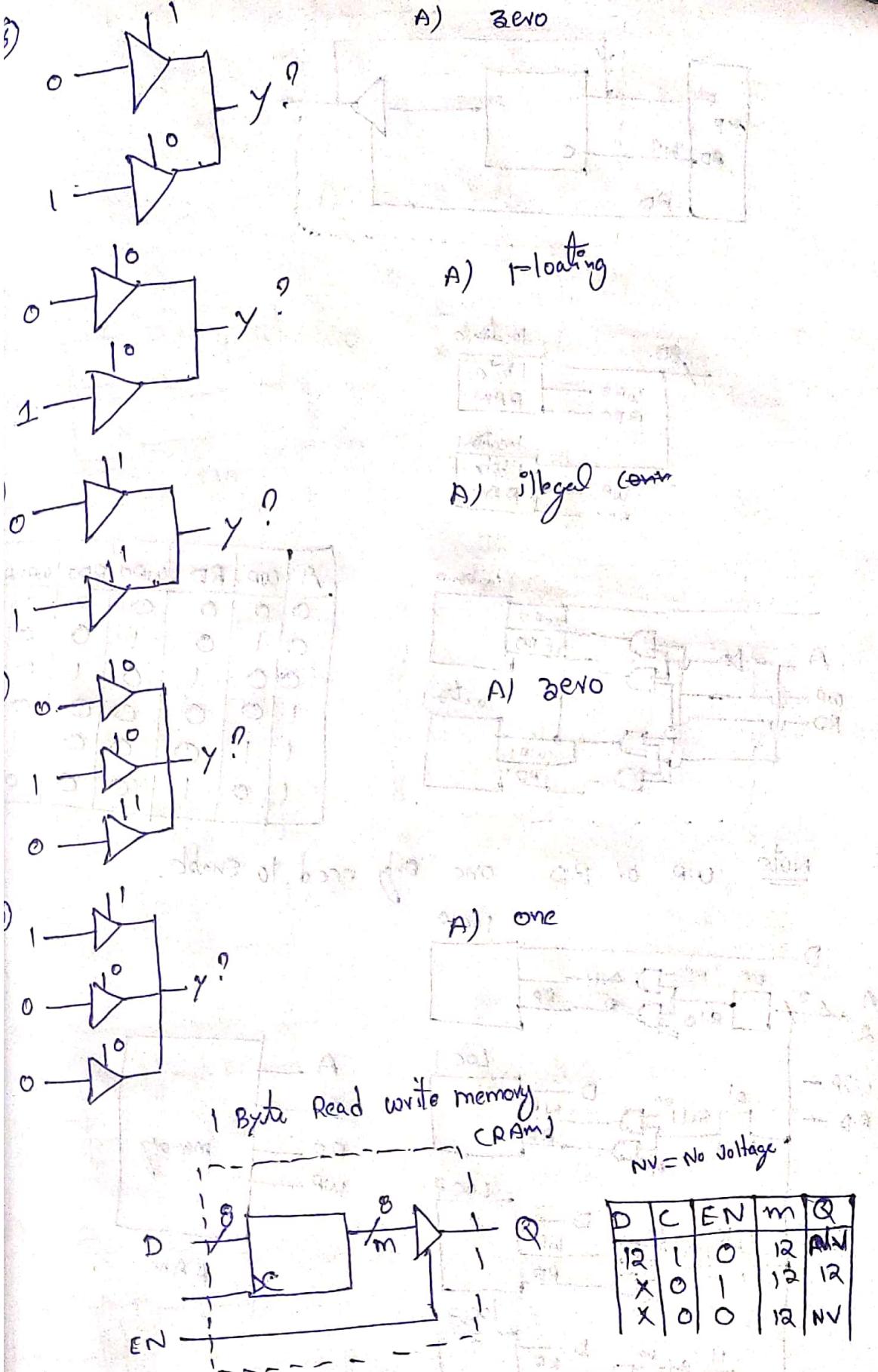


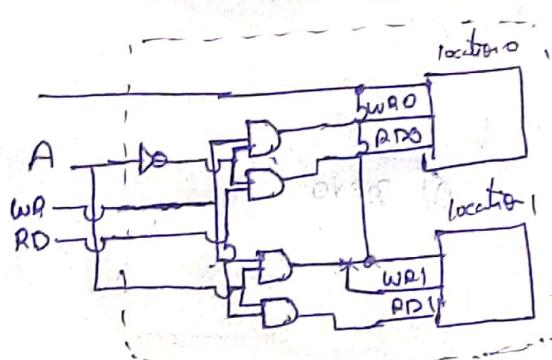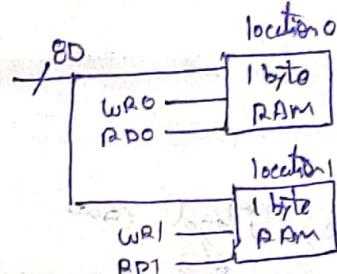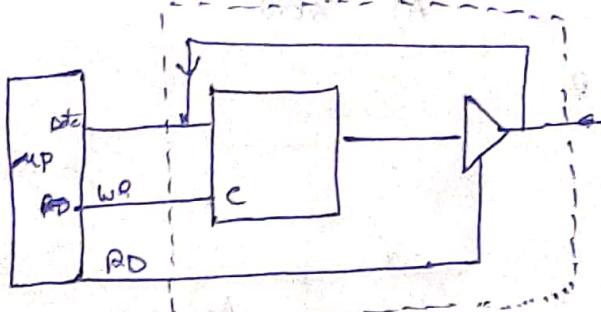
When  $C$  is 1 = write  
 $EN = 1$  = Read  
 $C = EN = 0$  = store



A	WR	RD	WR0	RD0	WR1 RD1
0	0	0	0	0	0 0
0	1	0	1	0	0 0
0	0	1	0	1	0 0
1	0	0	0	0	0 0
1	1	0	0	0	1 0
1	0	1	0	0	0 1


Note WR or RD one only need to enable.

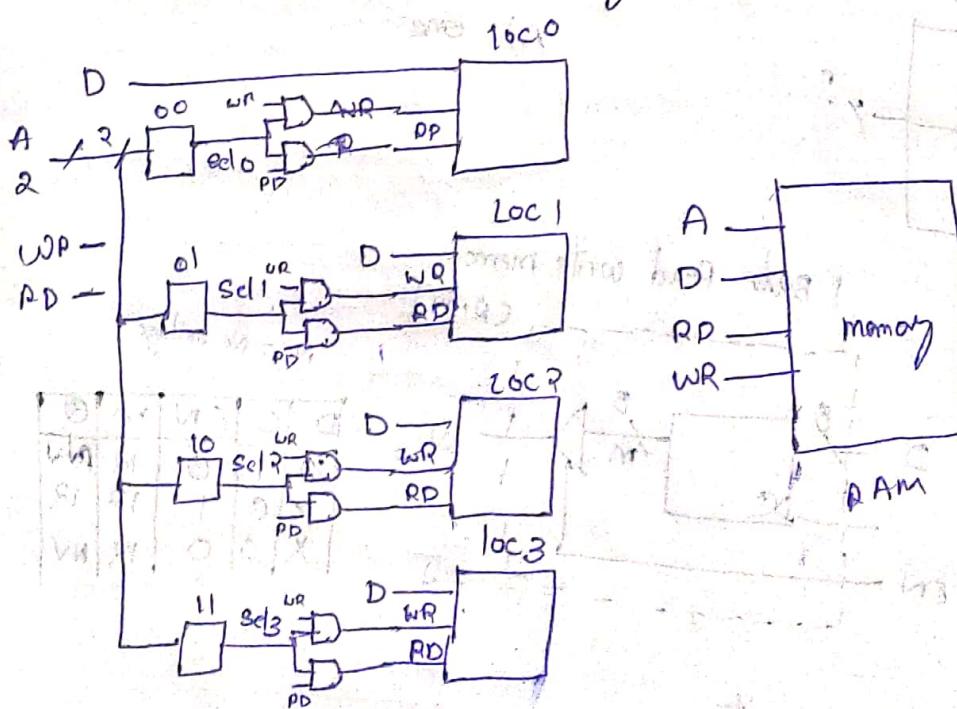

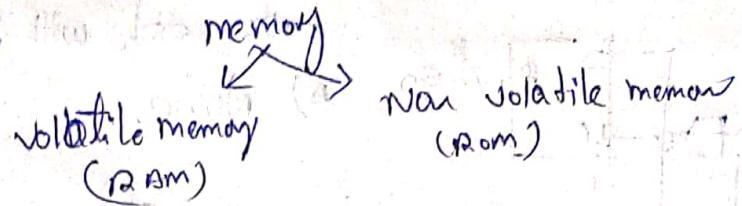


## RAM

## Assessment - 1

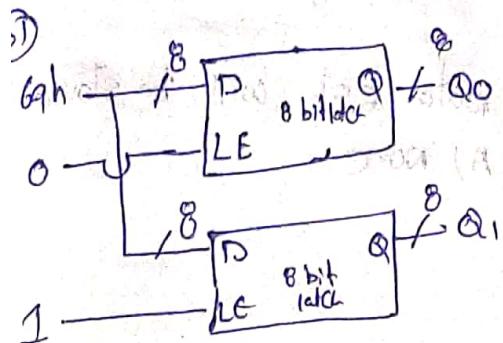


Data 69h will be stored in?

A) Q1

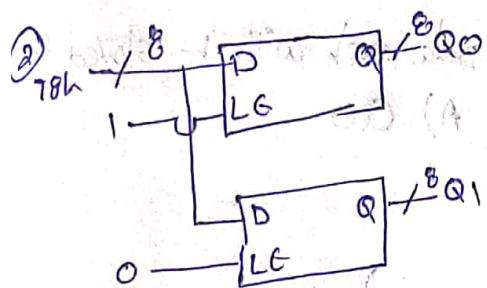


Data 78h will be stored in?

A) Q0

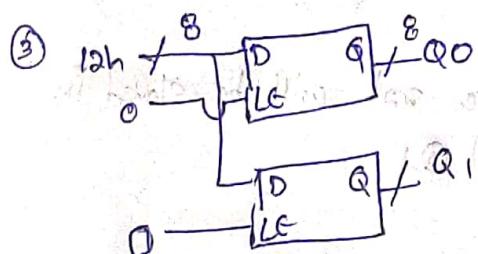


Data 12h will be stored in?

A) None

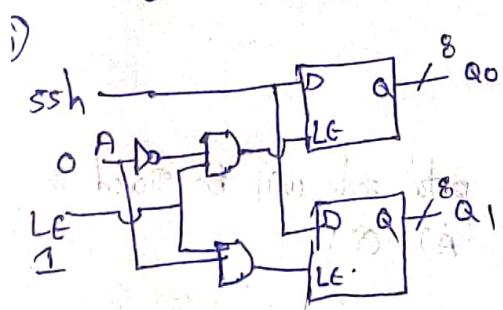


Data 55h will be stored in?

A) Q0

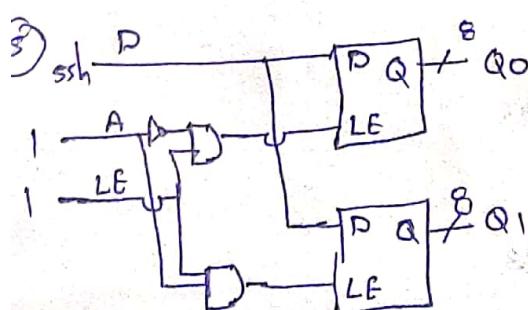


Data 55h will be stored in?

A) Q1

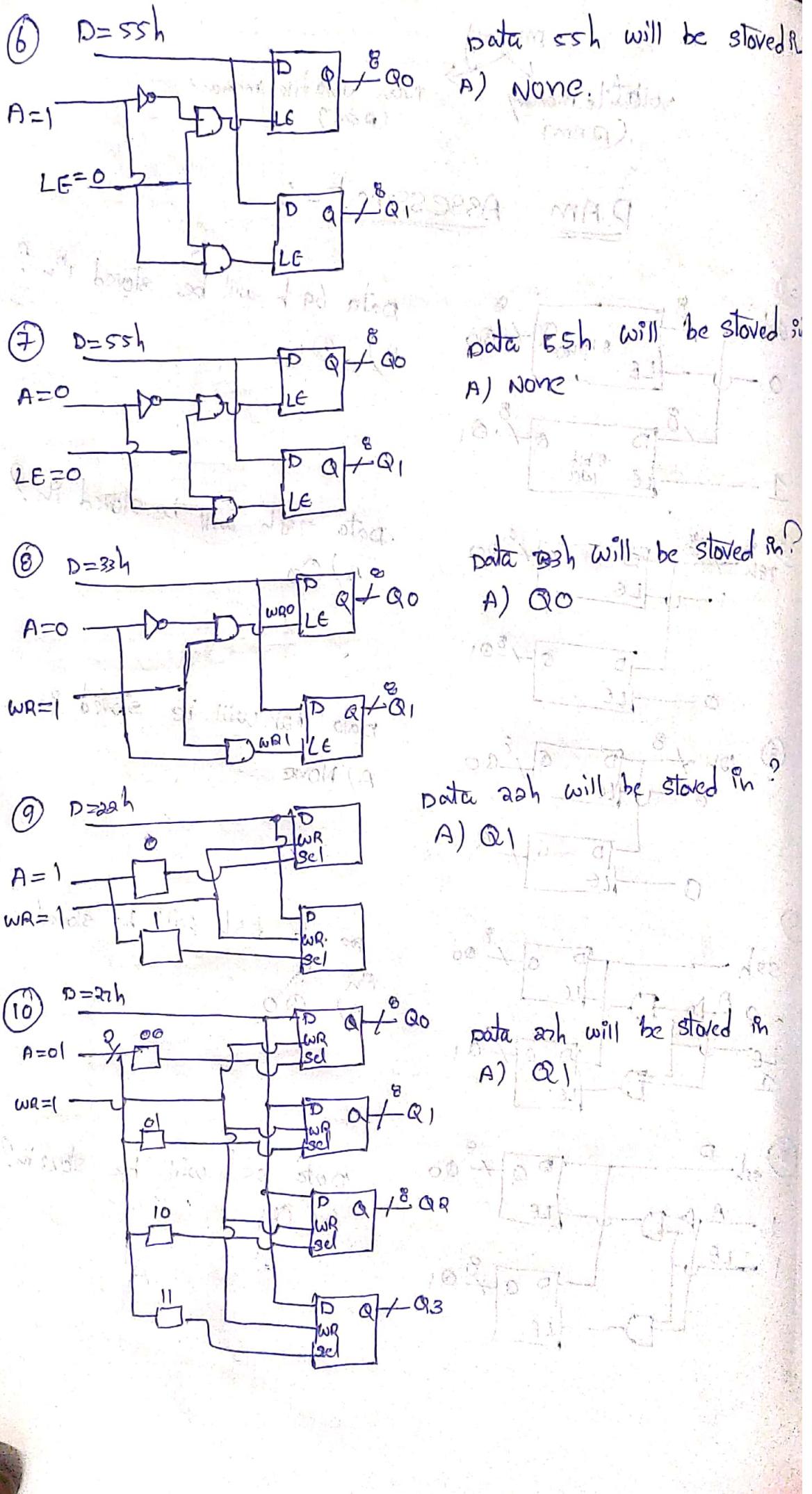


# RAM 2 Assessment


① 1 byte Read write memory RAM 1

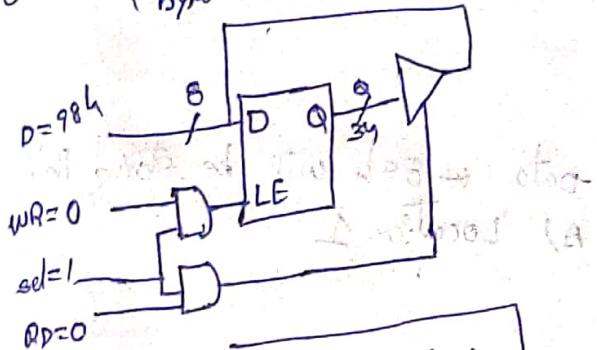


what is the value of Q?  
A) 3uh

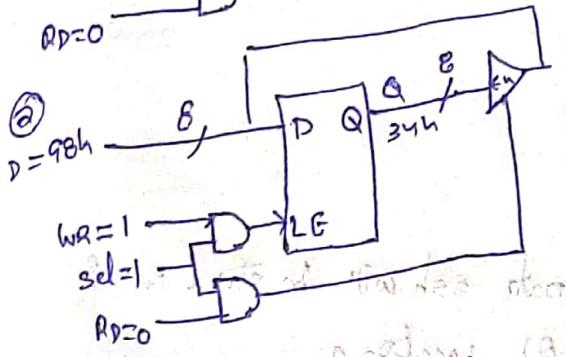


what is the value of Q?  
A) 98h

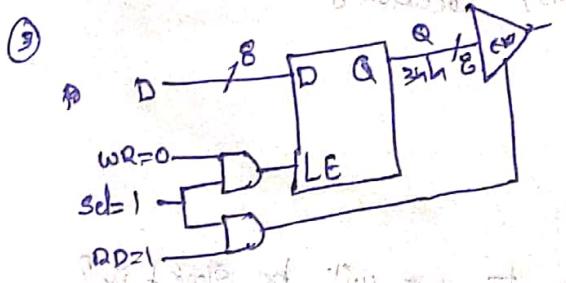


what is the value of D?  
A) 3uh

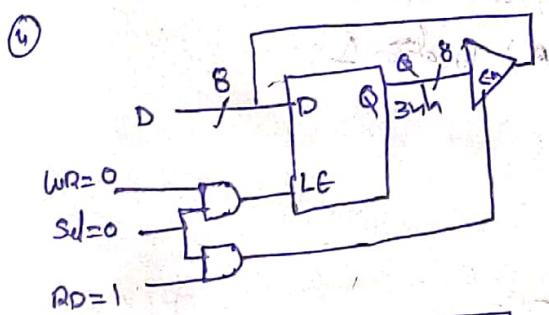


what is the value of Q?  
A) Floating

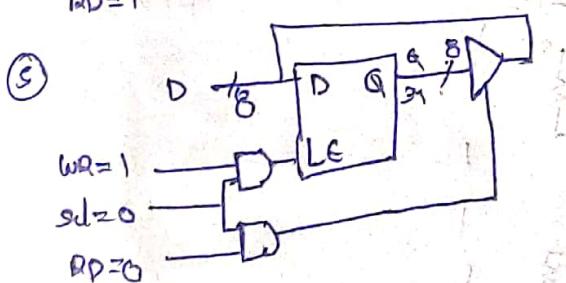

what is the value of Q?  
A) 3uh

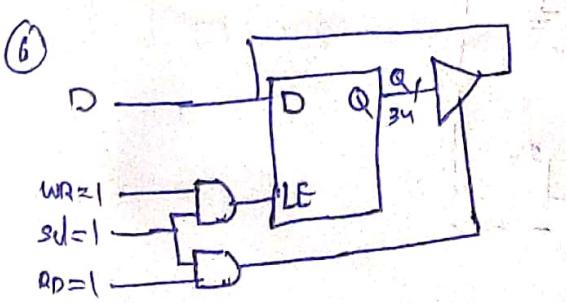


what is the value of Q?  
A) illegal

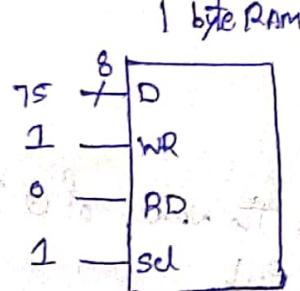


What is the value of Q?

- A) 75h

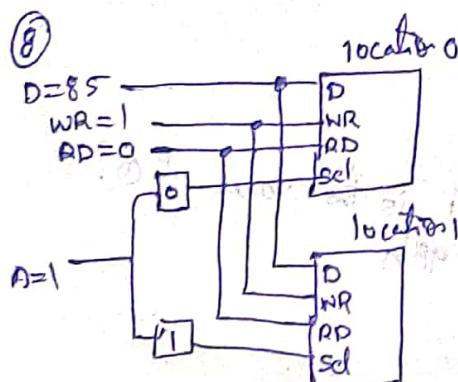


Data  $\leftrightarrow$  85h will be stored in?

- A) Location 1

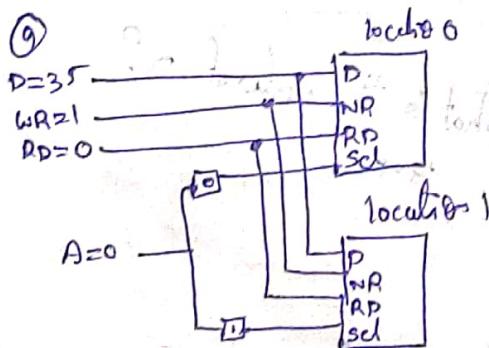


Data 35h will be stored in?

- A) location 0

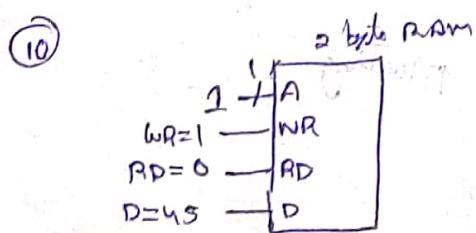


Data 45 will be stored in?

- A) location 1

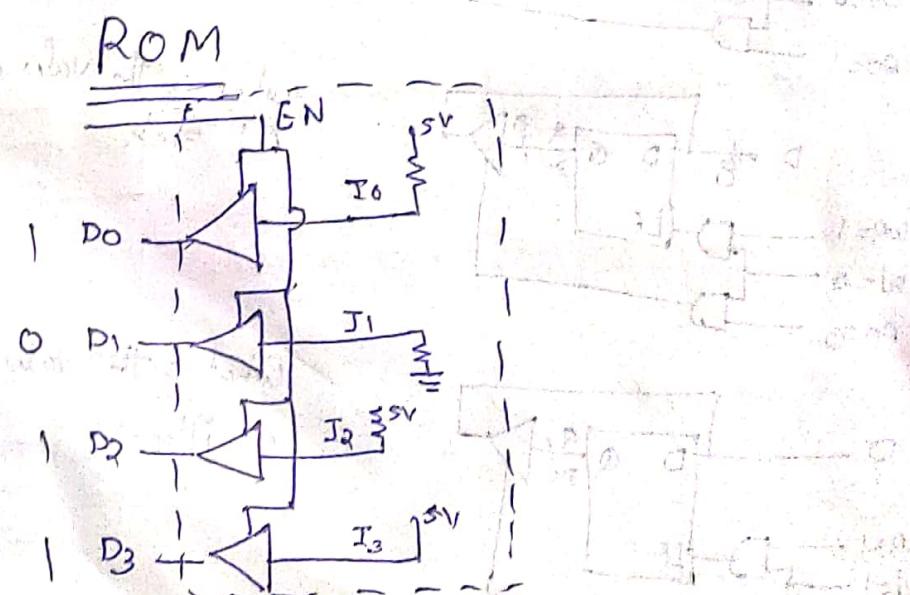

Read only memory  
(ROM)

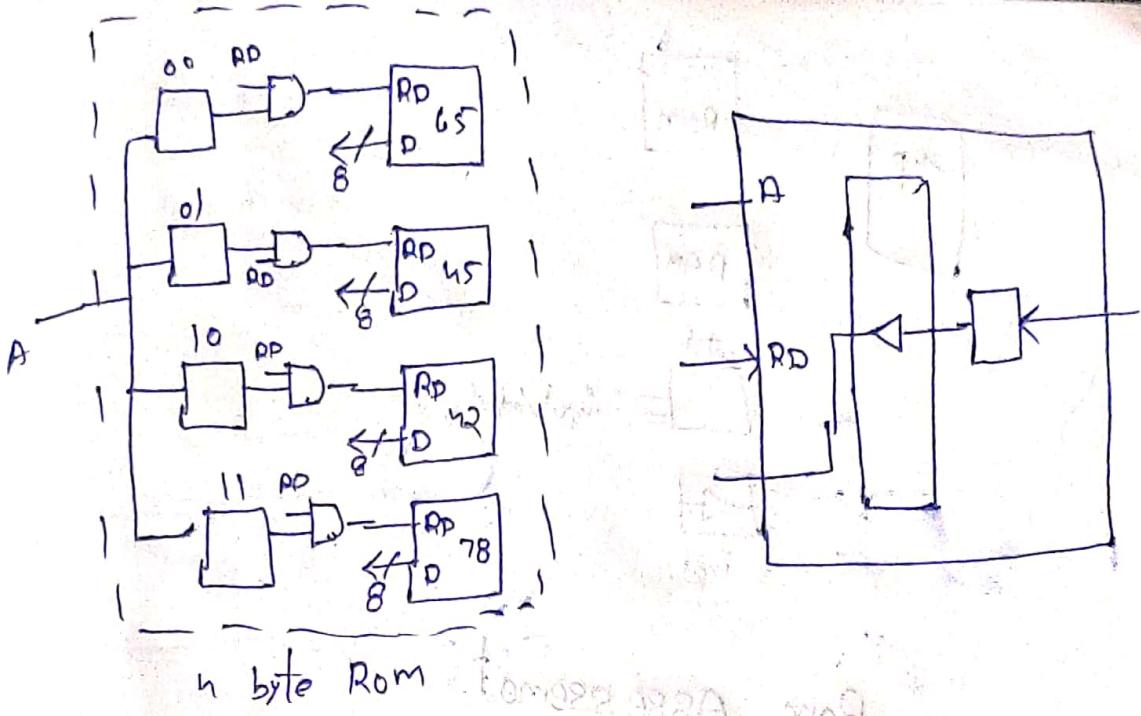

magnetic Rom - No charge

PROM - one time charge

EPRom - erasable programmable


EEPROM - electrically erasable

Flash - Block EEPROM

NOR NAND

magnetic Tape

read write head

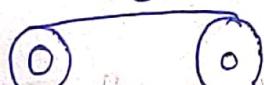

sequential Access memory (SAM)

memory

SAM

RAM

DRAM


ROM

EPRom


EEPROM

FLASH


NOR NAND  
(SD card  
pen drive  
etc.)

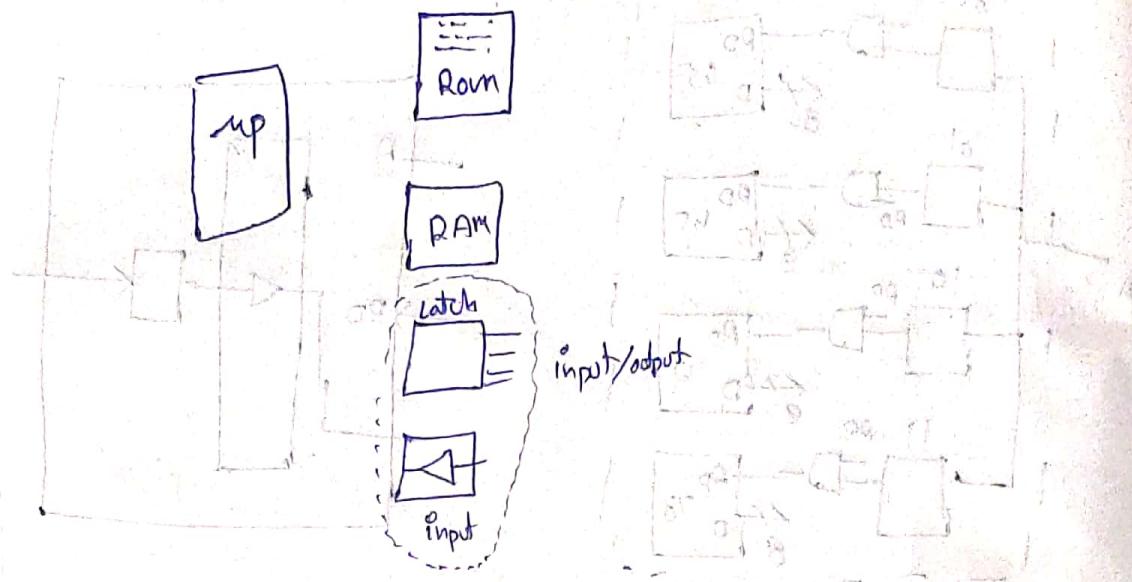


## Rom Assessment

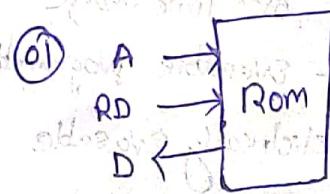


Rom is a Random Access memory

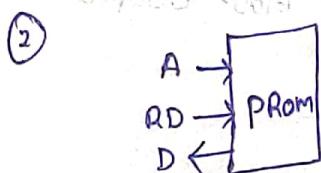


PROM is an one time programmable memory

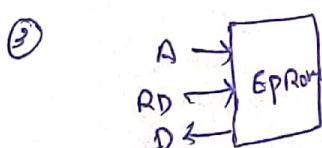


EEPROM is UV erasable memory

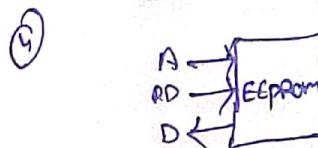

E2PROM is electrically erasable Rom

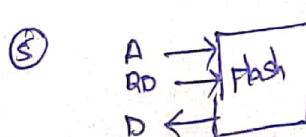


Flash is block electrically erasable Rom

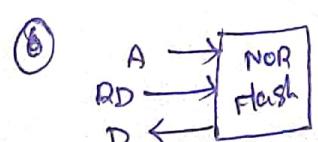


NOR flash is Random access memory




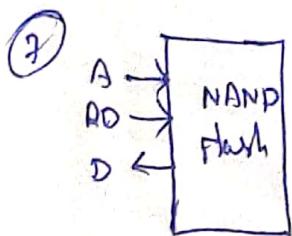

NAND Flash is sequential Access memory

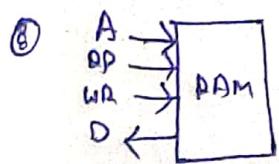

RAM is a Read write memory

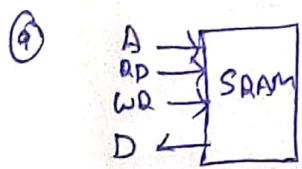

Read write memory



Read write memory